 


Digital Music Player ELEX7660 Digital System Design

Nathaniel Rohrick
Preston Thompson



Contents

1	Introduction	4
2	Background	5
2.1	Digital Audio	5
3	System Architecture	5
3.1	Digital-to-Analog Conversion	6
3.1.1	dac CPU Peripheral	7
3.1.2	Analog Front-End	7
3.1.3	Class-D Amplifier	7
3.2	SD Card Data Management	12
3.2.1	spi CPU Peripheral	13
3.3	sdc Driver for SD Card Using the spi Peripheral	14
3.4	keypad CPU Peripheral	16
3.5	keypad Driver	16
3.6	ledc CPU Peripheral	17
3.7	Firmware	17
3.7.1	SD Card Format	18
3.7.2	FAT32 Driver	19
4	Challenges	20
4.1	dac Ring Buffer	20
4.2	Keypad	20
4.3	SD Card	20
5	Conclusion	21
6	Appendice	23
6.1	QSYS Circuit Schematic	23
6.2	Class-D Amplifier Circuit Schematic	24
6.3	Software Listings	31
6.4	Bill of Materials	61
6.4.1	BOM billed to BCIT	61
6.4.2	Class-D Amplifier BOM	62

List of Figures

1	System block diagram	5
2	Breadboarded DAC circuit	6
3	DAC circuit schematic	6
4	Stereo PWM schematic	8
5	Single channel PWM output	9
6	Schematic of complementary PWM generator with deadtime	9
7	Single channel H-Bridge schematic	11
8	SD card circuit schematic	12
9	State-machine for <code>spi</code> peripheral	13
10	State-machine for the <code>keypad</code> peripheral	16
11	Flowchart of firmware's main loop	18
12	Class-D amplifier schematic pg. 1/6	25
13	Class-D amplifier schematic pg. 5/6	26
14	Class-D amplifier schematic pg. 3/6	27
15	Class-D amplifier schematic pg. 4/6	28
16	Class-D amplifier schematic pg. 5/6	29
17	Class-D amplifier schematic pg. 6/6	30
18	Components used in final design	61
19	Components needed for class-D amplifier	62

Listings

1	<code>musicplayer_top.sv</code>	31
2	<code>ledc.sv</code>	31
3	<code>dac.sv</code>	32
4	<code>dac_tb.sv</code>	34
5	<code>spi.sv</code>	36
6	<code>spi_tb.sv</code>	39
7	<code>sdc.c</code>	41
8	<code>sdc.h</code>	46
9	<code>sdc_cmd.h</code>	46
10	<code>keypad.sv</code>	47
11	<code>keypad.c</code>	50
12	<code>keypad.h</code>	51
13	<code>main.c</code>	51
14	<code>fat.c</code>	53
15	<code>fat.h</code>	55
16	<code>deadtime.m</code>	56
17	<code>V12switcher.m</code>	56
18	<code>GATE_DRV_DESIGN.m</code>	59

1 Introduction

For our Digital System Design course at BCIT we decided to build a digital music player. The system reads digital audio off of an SD card and interfaces to a digital-to-analog converter. While this certainly has been done before (every cell phone sold today is capable of this!) we wanted to design the digital hardware from scratch and learn about SD cards and digital audio.

In addition, we started work on a class-D audio amplifier to go along with the digital music player. The inspiration originally was to have the FPGA drive the H-bridge of the audio amplifier directly however we found out that the speed requirements to do this digitally were not possible. In light of this, the amplifier became a side project of the music player. We have included it in this report for posterity.

Work was also started on a FAT32 firmware driver and but due to time constraints it was not integrated with the rest of the system.

2 Background

2.1 Digital Audio

The audio format used in this project follows the Compact Disc Digital Audio (CDDA) standard for audio stored on CDs. The audio encoding used is 2-channel signed 16-bit PCM with a sample rate of 44.1 kHz. For simplicity, we opted to use little endian byte ordering to store the samples as the Nios II processor is little endian.

The music used to demonstrate this project came originally from MPEG-3 encoded audio files (.mp3). The MPEG-3 audio first needed to be decoded for use with the music player. To do this, a Linux utility (`mpg123`) was used to decode the audio and save it in the Waveform Audio File Format (.wav). Afterwards, another Linux utility (`sox`) was used to convert the .wav files to the raw audio format described above.

3 System Architecture

The system consisted of a Nios II soft-core processor and three custom memory-mapped peripherals for it: the `dac`, the `spi`, the `keypad` and the `ledc` modules.

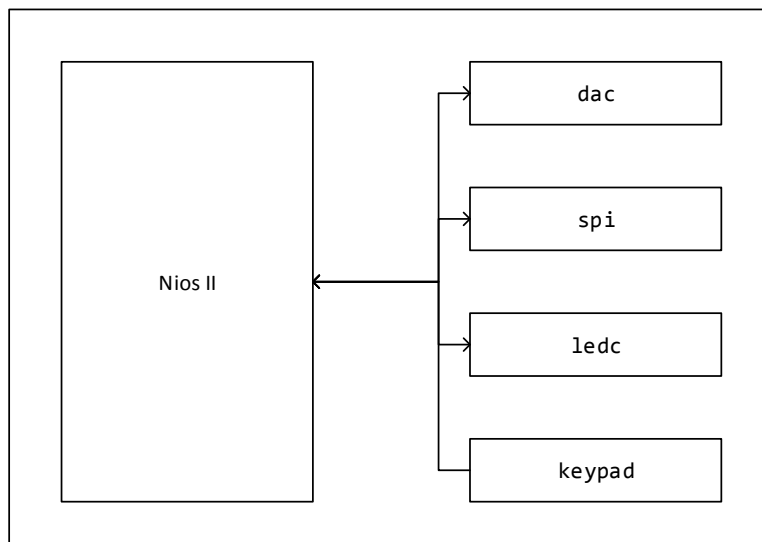


Figure 1: System block diagram

3.1 Digital-to-Analog Conversion

 


Figure 2: Breadboarded DAC circuit

The DAC used is a Burr-Brown PCM1725 Stereo Audio 16 bit 96 kHz DAC. The DAC only came from Digikey in a SOIC-14 package, so a SOIC-14 breakout board from Adafruit was used to connect it to the breadboard.

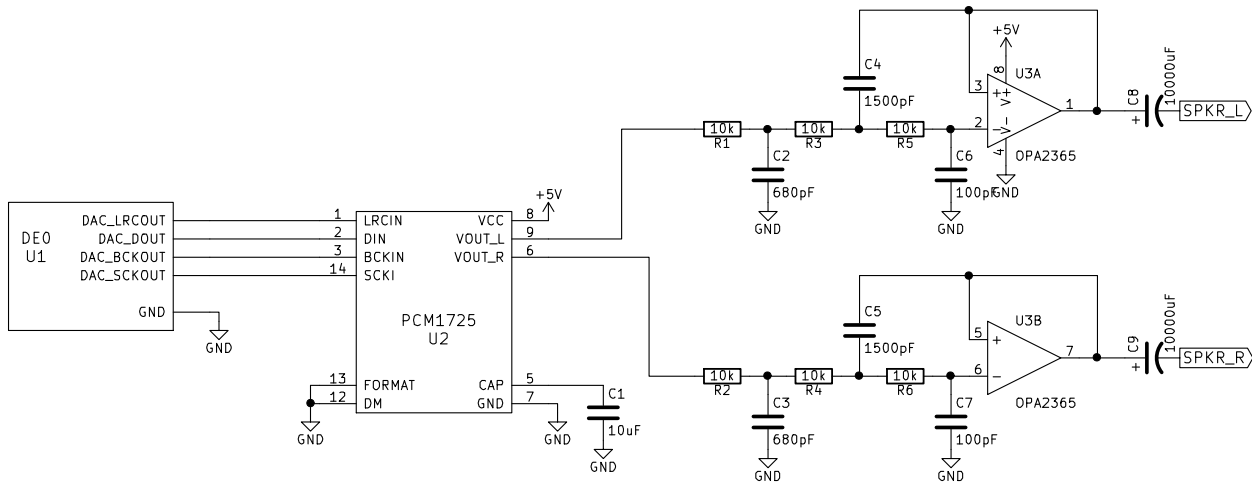


Figure 3: DAC circuit schematic

3.1.1 dac CPU Peripheral

The PCM1725 DAC supports I²S as well as having its own digital interface described in its datasheet. Fortunately this digital interface is simple enough to be able to interface to using nothing but the timing diagram. The only detail that was not mentioned in the datasheet is that the DAC uses signed integers.

A complication we faced was that the sample rate of the music was not an integer divisor of the FPGA's system clock. Even using one of the available PLLs on the FPGA would not get an accurate enough clock because of the large multiplier and divisor. To solve this problem, we devised a method where the DAC chip's clock signal's period was constantly modified to average out to make exactly 44.1 kHz playback rate.

The `dac` peripheral has a FIFO in the form of a ring buffer for storing the samples. From the CPU's perspective there is only one register to write to, `dac_sample`. When the CPU writes to `dac_sample`, the `dac` peripheral puts the sample onto the ring buffer. The format of the data written to `dac_sample` is the 16-bit left channel sample in bits [31:16] and the 16-bit right channel sample in bits [15:0].

3.1.2 Analog Front-End

The output of the DAC needed to be filtered, amplified, and AC-coupled before going out to a pair of headphones or speakers. To do this we used an audio-grade op-amp, the OPA2134PA. It is a dual op-amp circuit in a DIP-8 package. The op-amp was configured to be a 3rd order low-pass filter. The output of the op-amp is AC-coupled before connecting to a 3.5mm TRRS stereo connector.

3.1.3 Class-D Amplifier

The class-D amplifier is a power amplifier topology that boasts the highest power efficiency of all the amplifier classes. It accomplishes this by modulating the input signal to a high frequency pulse-width modulated waveform (PWM). Since PWM is digital in nature, they do not require FETs to be in the linear I-V region. FETs dissipate little power in the saturation conduction region and efficiency is mostly limited by switching losses [1].

To modulate the incoming signal, a simple comparison is made with a triangle wave which acts as the carrier. Below gives a practical implementation of this modulation scheme [2].

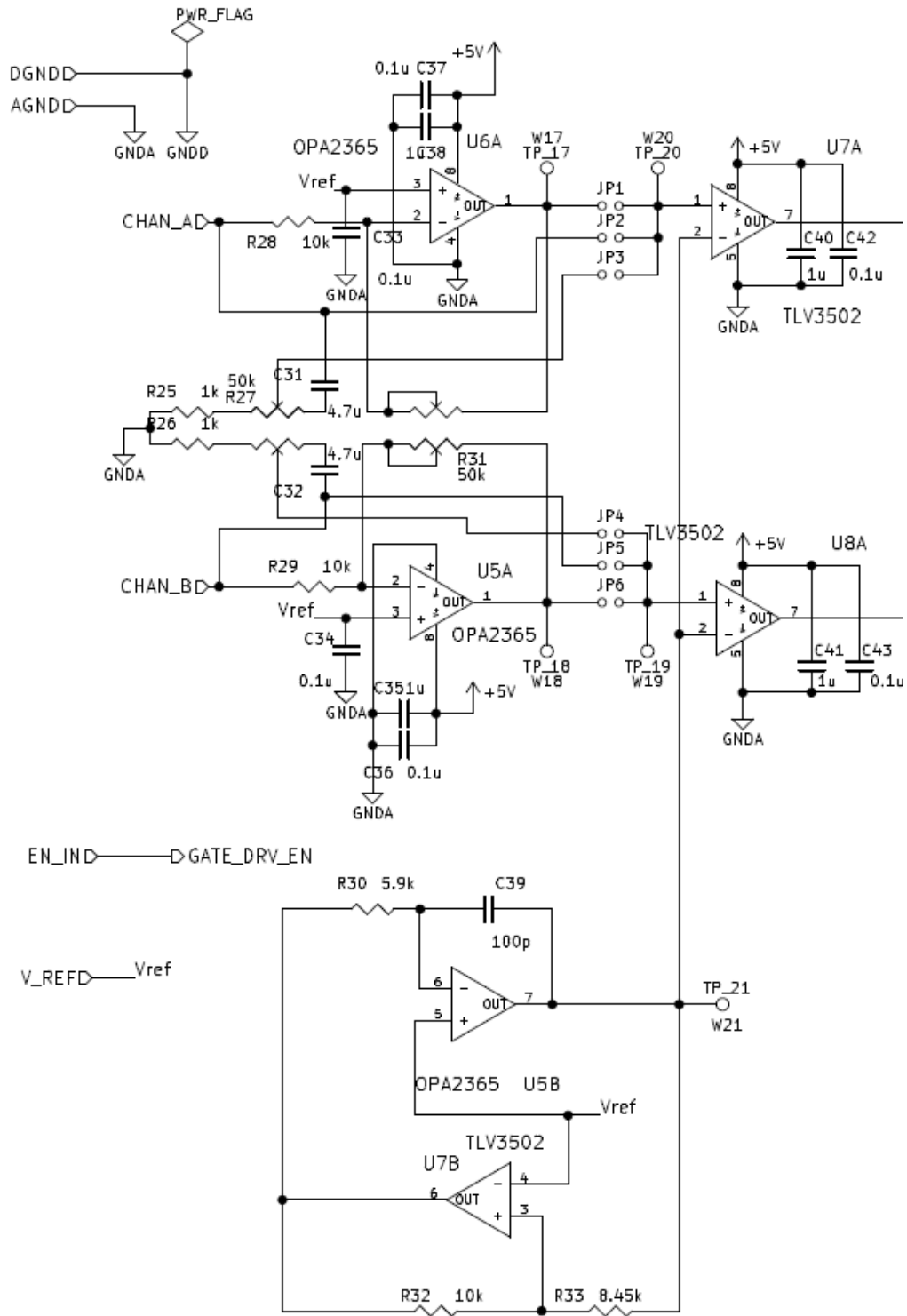


Figure 4: Stereo PWM schematic

 


Figure 5: Single channel PWM output

Now we have a digital signal that represents the baseband signal's amplitude in its duty cycle. From this signal, we can drive an inverter topology of our choosing. In this case we've selected the H-bridge topology for higher power amplification for a given supply voltage. Before we can do this, we need complementary PWM signals with deadtime. This is accomplished with a simple inverter and a FET based asymmetric RCD delay network fed into a comparator with hysteresis. Below shows such a circuit, its complement has an inverter at the input.

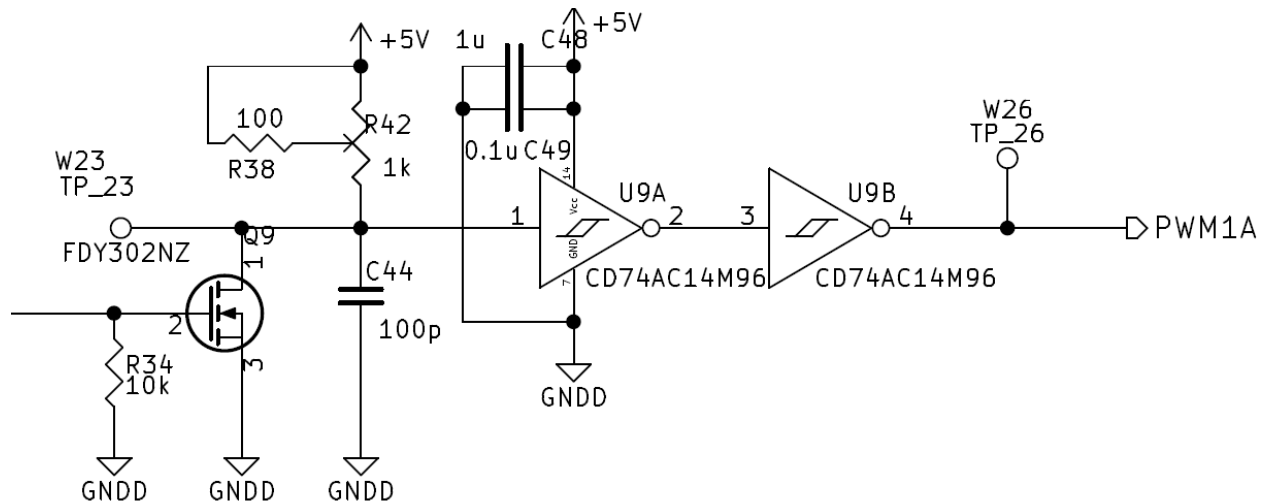


Figure 6: Schematic of complementary PWM generator with deadtime

Lastly, the power stage of the amplifier. The H-bridge is constructed of 4 FETs controlled by PWM. For stereo audio we would require a total of 8 FETs! Some unique challenges are faced by the designer; particularly, driving the relatively large gate capacitances of the FETs

at high frequencies and driving the floating gate of the high side FET. Information can be found at [2]. This is left to the reader to analyze and is out of the scope of this report. A single channel of our design can be seen on the next page.

Demodulation is accomplished by simply filtering off the carrier frequency. In our case it was recommended by [2] to use a second order Butterworth filter with only reactive components to minimize losses.

Additional electronics was needed for the operation of this all-in-one class-D amplifier, particularly the power supply designs, input protection and signal conditioning, jack detect, and DC blocking. Appended to the end of this report is the complete schematic. MATLAB scripts developed for the analysis of the design are also included.

11

PWM1AD — PWM_1_A
PWM1BD — PWM_1_B

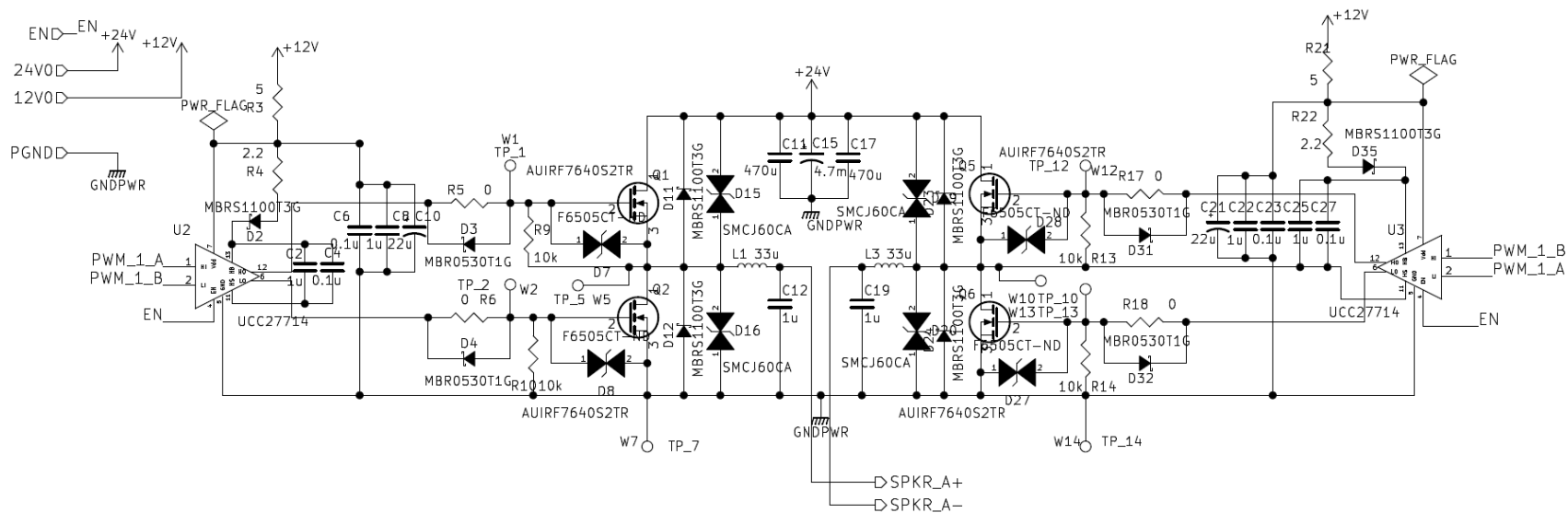


Figure 7: Single channel H-Bridge schematic

3.2 SD Card Data Management

For the implementation of the music player we require a music source to play from. A significant amount of data storage is necessary for this project because we won't have the means to decompress MPEG-3 encoded audio. Therefore we will be using raw 16-bit signed audio with a sample rate of 44.1 kHz. This will also put considerable strain on the communications interface and CPU when managing the immense amount of data.

The SD card interface will be broken down as follows:

- Hardware communications interface `spi.sv`
- Firmware driver for communications interface `sd_card.c`
- The main loop in `main.c`

The SD card used is the SDHC variant card which allows for capacities up to 32GB. We will be utilizing a micro SD card breakout board by Adafruit which will be powered and controlled by the DE0 Nano.

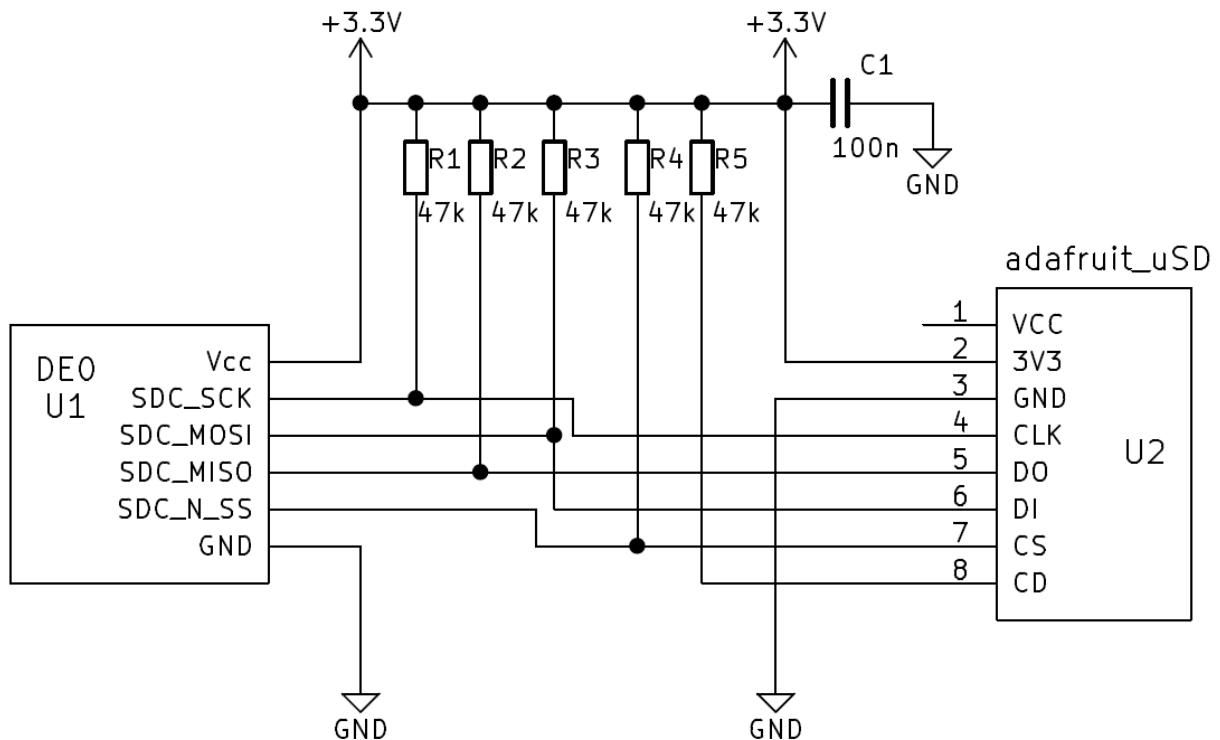


Figure 8: SD card circuit schematic

Below we will detail the requirements and design steps needed to realize the above components of the SD card interface.

3.2.1 spi CPU Peripheral

SD cards can be communicated with using two protocols: a serial peripheral interface (SPI) and a proprietary 5 wire synchronous communications interface. We will be using SPI since the latter requires licensing from the SD Association. From [3], the SD card requires the following hardware parameters:

- Variable SCK control
- 8-bit data packets
- Type 0 SPI mode
- Send and receive capability
- Busy status flag
- CPU integratable

Because we have incorporated the Nios II softcore processor in our design, it allows us to have direct control over our `spi` peripheral by connecting control registers to the Avalon MM bus. Given the CPU's ability to read/write to data registers, we can set status flags for the CPU to check and data/control registers to operate the `spi` peripheral.

The entire `spi` peripheral can be broken down into 3 states represented below as a state diagram:

 


Figure 9: State-machine for `spi` peripheral

At start-up the module enters the `init` state which initializes all the design registers and settings to a default value. This involves setting a `clk` divider to 2 (max `sck` speed) and pre-loading the corresponding counters to drive `sck`.

Additionally, any state (including `init`) will transition to `init` when the `reset` signal is asserted. After a single `clk` cycle the state machine transitions to `idle` where the peripheral is continuously loading valid count and I/O pin states, as well as handling CPU requests to read/write data to its registers.

When the CPU requests to write data to the `rcv_buf` the next state becomes `snd_rcv`. This state pulls the busy flag high and sends/receives data through the `mosi` and `miso` signals. This is accomplished using a shift register designed using pointer arithmetic in hardware. When exactly 8 falling edges of `sck` have been sent over `mosi`, the next state becomes `idle` and the busy flag is deasserted.

3.3 sdc Driver for SD Card Using the spi Peripheral

To simplify the configuration of the `spi` peripheral and initialization process of the SD card, we opted for a firmware solution for this task. We've developed an API for the SD card constituting the following functions:

- `bool sdc_init();`
- `bool baud_set(uint8_t div);`
- `bool sdc_read(uint32_t addr, uint8_t len, uint8_t* const buf);`
- `bool sdc_send_cmd(const uint8_t cmd, const uint32_t payload, const uint8_t resp, uint8_t* const resp_buf);`

The `baud_set()` function takes an argument `div` and simply checks whether the `spi` interface is busy by parsing the busy flag, if not busy the CPU writes `div` to the divider register in the `spi` peripheral.

The `sdc_send_cmd()` follows a command and response sequence specified by the SD card specification found in [3]. It starts by pulling `n_ss` line low and sends a command byte, a 4 bytes payload, and a CRC byte over `mosi`. The CRC byte is optional in SPI mode according to [3]. This function then commands the `spi` peripheral to send dummy bytes (0xFF) to shift data in from the SD card over `miso`. The beginning of a response is indicated by a start bit. Once a response is received, it checks if the command was accepted and if the SD card is functioning properly.

The SD card always responds to a command with a defined response which can vary between different commands. The exact expected response has to be specified by the caller but could conceivably be decoded with a simple lookup table.

The initialization function `sdc_init()` initializes the sd card following the procedure outlined by [3]. It utilizes the `sdc_send_cmd()` and `baud_set()` functions to operate.

Finally the `sdc_read()` function is used to read a set amount of blocks from the SD card. It takes an address, expected length of response in blocks and a pointer to a buffer to put the data into. This function utilizes `sdc_send_cmd()` to initialize the data read then iterates a loop that loads the response into `buf`. We will be transferring the contents of `buf` into the `dac` ring buffer.

3.4 keypad CPU Peripheral

We required a means for the user to control audio playback. We designed a **keypad** module that detects a keypress and decodes the value and stores it into a register that can be read by the CPU. The internal circuitry of the keypad is a 4x4 matrix of normally open switches with each row and column connected to a pin header. We set up the DE0 to output to the rows and have the columns connected as inputs with pull-up resistors enabled. To decode a keypress we simply pull a row low and check the states of the columns. If any of the column are low, continuity to ground has been made and the exact button pressed can be determined from the low row/column combination.

To ensure reliability a hardware debouncer was setup to store the decoded value on the positive edge of clk immediately after a keypress is detected then wait 100 ms before checking again. The state machine is illustrated below:

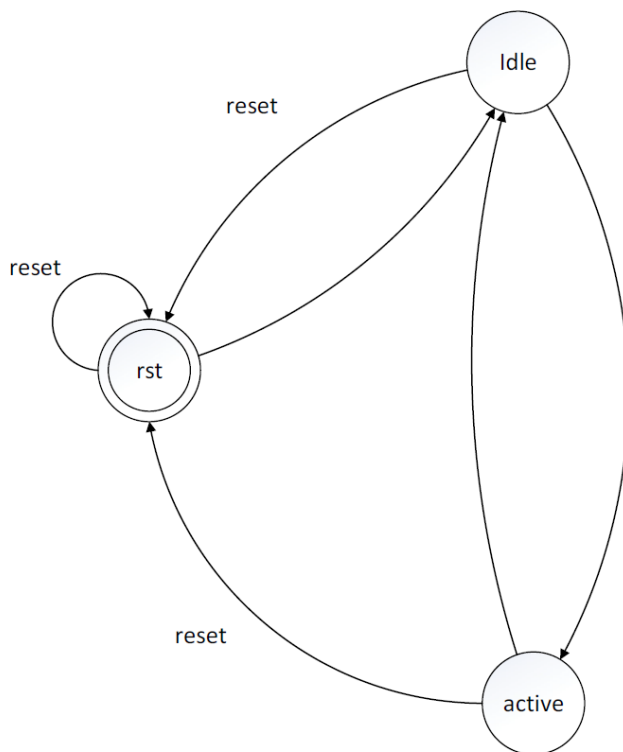


Figure 10: State-machine for the keypad peripheral

3.5 keypad Driver

A simple API was created for the **keypad** module, the `keypad_get_button()` function, which parses the register that stores the latest keypress and returns an integer corresponding to the key pressed. An enumeration is defined in a header file that details the return value. This module is designed such that the main program should constantly be polling with this function to detect any changes in keypress states. The physical hardware configuration is as simple as connecting the 8 pin headers to the keypad board.

3.6 ledc CPU Peripheral

The `ledc` is the LED controller peripheral. Initially it was designed to control the LEDs on the DE0 Nano board for debugging use, however later the `ledc` was extended to include GPIO functionality. The GPIO functionality made debugging much easier by allowing us to trigger an oscilloscope on events originating in firmware, and allowing us to determine the execution time of firmware subroutines.

3.7 Firmware

The firmware for the music player consisted of an initialization routine and a main program loop that checks the keypad for events, transfers audio data to the `dac` if there is room and handles switching to the next track if the currently playing track has reached its end.

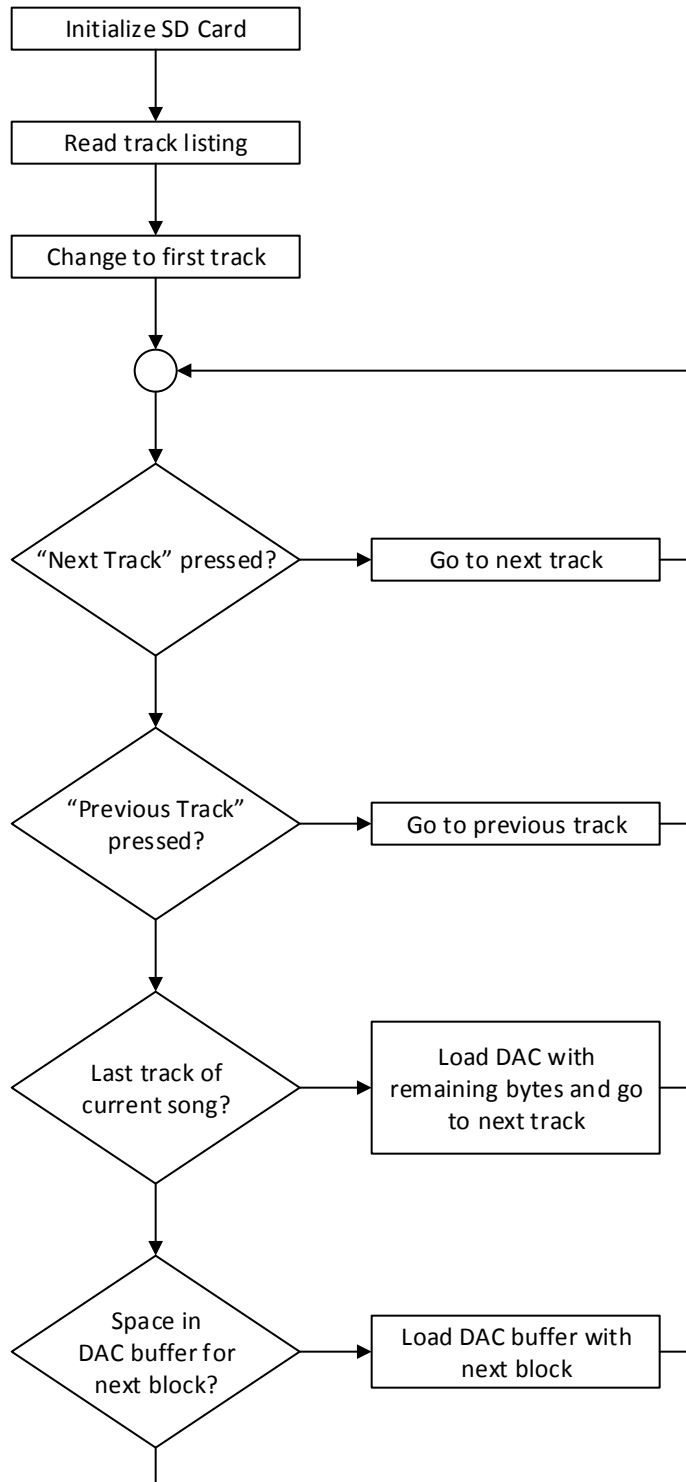


Figure 11: Flowchart of firmware's main loop

3.7.1 SD Card Format

After the music has been prepared as raw audio files, a Python script running on a Linux PC is used to prepare the SD card image. At the beginning of the image, in the first block (512

bytes), a table exists that contains information for each of the music tracks. For each track two pieces of information is recorded in the table: the file size in bytes, and which 512-byte block the track starts in. Finally, the UNIX utility `dd` is used to write the image to the SD card.

Each track starts on its own block. The space in between tracks is padded with zeros until the next track starts on a 512-byte block boundary. Below is an example of the SD card layout for two tracks.

Byte address	Description
0x0000	Track 0 start block number
0x0004	Track 0 size
0x0008	Track 1 start block number
0x000c	Track 1 size
0x0010	Zeros
...	
0x0200	Beginning of track 1
...	
0x29f4	Last byte of track 1
0x29f8	Zeros
...	
0x2a00	Beginning of track 2

3.7.2 FAT32 Driver

A basic read-only FAT32 implementation was created but due to time constraints it was not integrated into the project. It is capable of getting a directory listing of the root directory and reading files in the root directory. It is a primitive driver and is not optimized for performance. The source code listing is attached in the appendice section.

An important performance improvement that could be made for the FAT32 driver is to store the FAT in RAM instead of constantly re-reading the FAT to find out where the next sector of a file is.

4 Challenges

4.1 dac Ring Buffer

During initial debugging, we experimented with changing the `dac`'s FIFO buffer size. To do this, two things must be changed: the size of the `dac` buffer, and the limits of the read and write pointers for managing the ring buffer. In increasing the size of the `dac` buffer, we had to increase the limits of the read and write pointers. Once the initial issues had been resolved, we reduced the `dac` buffer size but forgot to change the limits of the read and write pointers.

The symptoms were that the audio would repeatedly click and stutter. This is because the write and read pointers that are supposed to index samples in the buffer were pointing beyond the limit of the buffer. Eventually the pointers would overflow and point within the buffer again and audio would resume properly.

To debug this issue, we created a GPIO module that allowed the CPU to toggle pins from firmware. By correlating the toggling of the pins with the audio glitches we were able to determine where the CPU was spending most of its time. This allowed us to rule out the SD card as the source of the glitches and revealed that the bug was in the `dac` module.

4.2 Keypad

During the initial bring-up phase of the `keypad` module we had much difficulty in getting all the rows to work on the keypad. After exhausting all other options over the course of several hours we finally decided to do a continuity test on the ribbon cable that connects the keypad to the FPGA. It turned out that one of the wires was broken. Continuity testing is important when using cheap ribbon cables.

4.3 SD Card

After all of our modules were designed and debugged, we encountered performance issues when reading information from the SD card. The maximum `sck` rate that we could reliably operate the SD card at was 12.5 MHz. Without a dedicated DMA module we optimized the firmware to improve efficiency on the firmware side. The minimum required baud rate needed to run 16-bit stereo audio is 1,411,200 bits per second. While this is significantly slower than SCK, the SD card latency coupled with ferrying uncompressed audio data with less than optimal code was introducing too much overhead. This was giving us a baud rate of 1,120,000 bits per second.

The solution was to simplify low level loops and pre-calculate constants used for the duration of the loop. Additionally, we increased the compiler optimization settings to maximum. With these changes the data rate exceeded 3,840,000 bits per second!

5 Conclusion

Overall, we saw many fine examples of digital system design. We learned more than expected. The `sdc` implementation proved to be the most complex module of the project. Overall, the project was a success and concluded with a working demonstration to the rest of the class.

Initially we were concerned about signal integrity issues surrounding the connection between the FPGA and the DAC and SD card. While error rates at 25 MHz were unacceptable, it not an issue at all at 12.5 MHz. Poor signal integrity would have limited our bitrate and potentially caused the whole project to fail if it was not fast enough. In our testing we did not detect any bit errors at this speed, although they could have been possible.


Recommendations for future work include finishing and validating the FAT32 filesystem implementation, implementing a real-time LCD-based frequency spectrum display, implementing an audio equalizer for boosting and attenuating frequency bands, and construct the class-D amplifier.

References


- [1] 2017. [Online]. Available: <http://www.irf.com/product-info/audio/classdtutorial.pdf>
- [2] 2017. [Online]. Available: <http://www.ti.com/lit/ug/slau508/slau508.pdf>
- [3] F. Foust, "Secure digital card interface for the msp430," 2017. [Online]. Available: http://alumni.cs.ucr.edu/~amitra/sdcard/Additional/sdcard_appnote_foust.pdf
- [4] Terasic Inc, "De0 nano user manual," 2017.
- [5] E. Casas, "Digital system design," 2017.

6 Appendice

6.1 QSYS Circuit Schematic

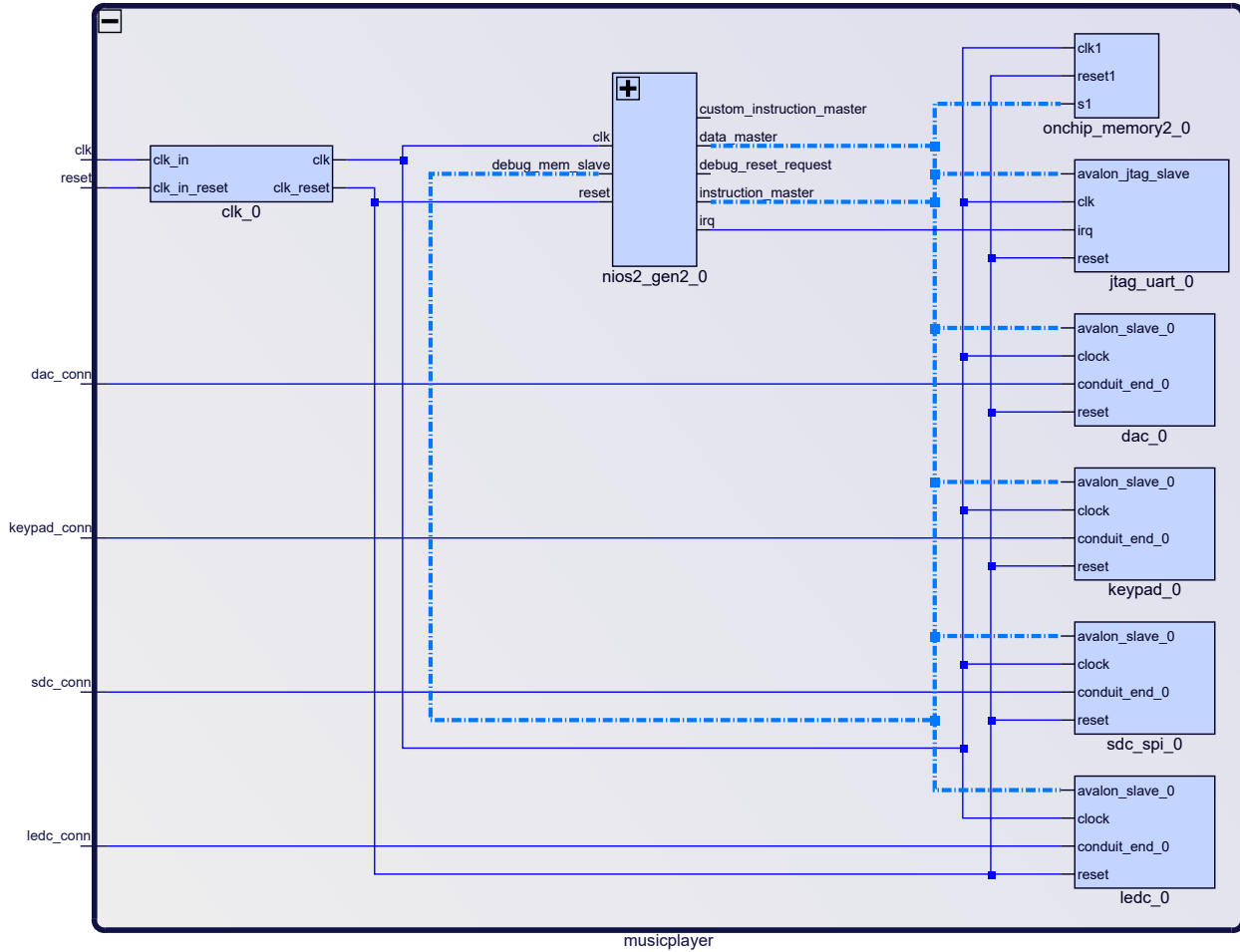

6.2 Class-D Amplifier Circuit Schematic

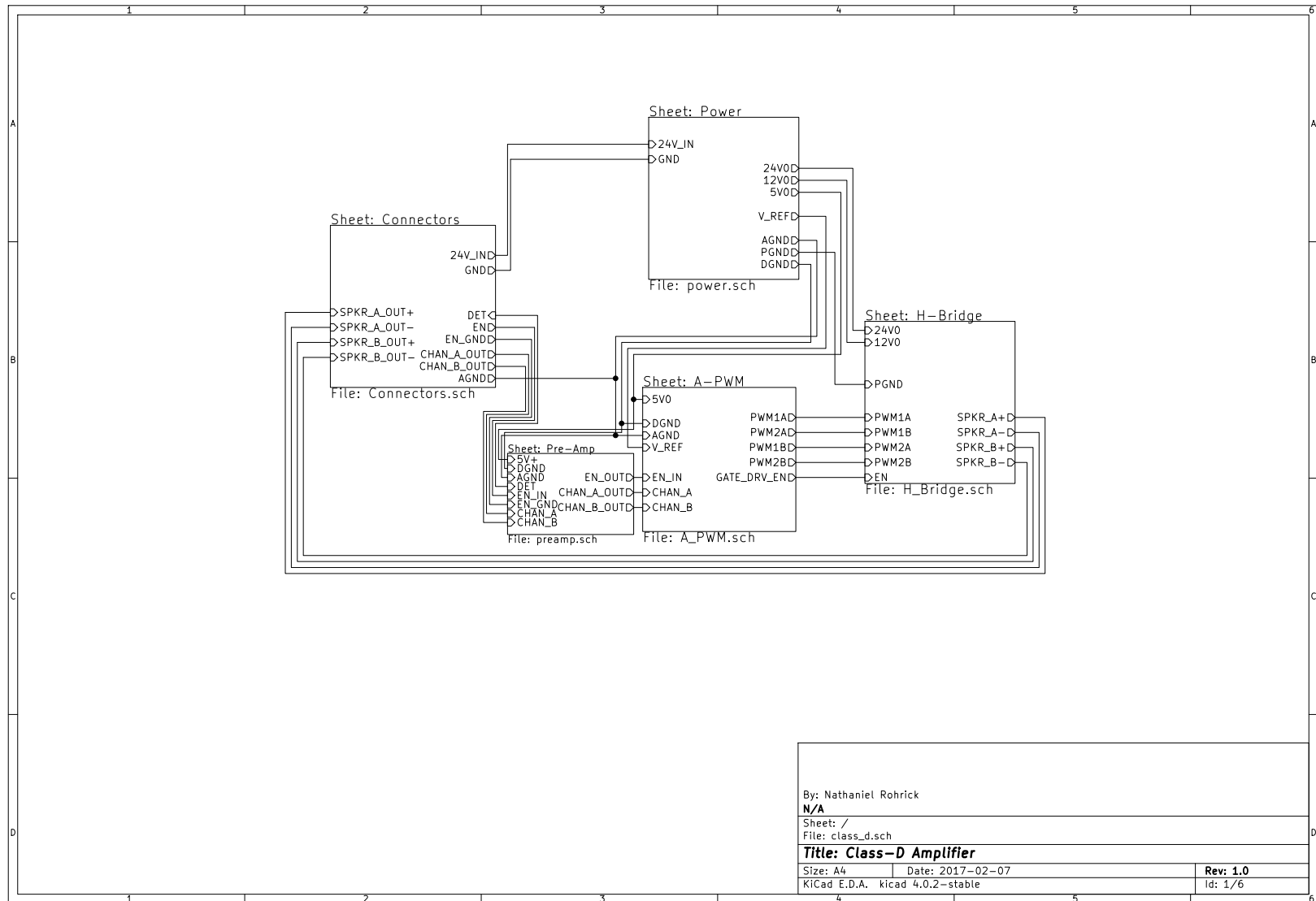

By: Nathaniel Rohrick		
N/A		
Sheet: /		
File: class_d.sch		
Title: Class-D Amplifier		
Size: A4	Date: 2017-02-07	Rev: 1.0
KiCad E.D.A. kicad 4.0.2-stable		Id: 1/6

Figure 12: Class-D amplifier schematic pg. 1/6

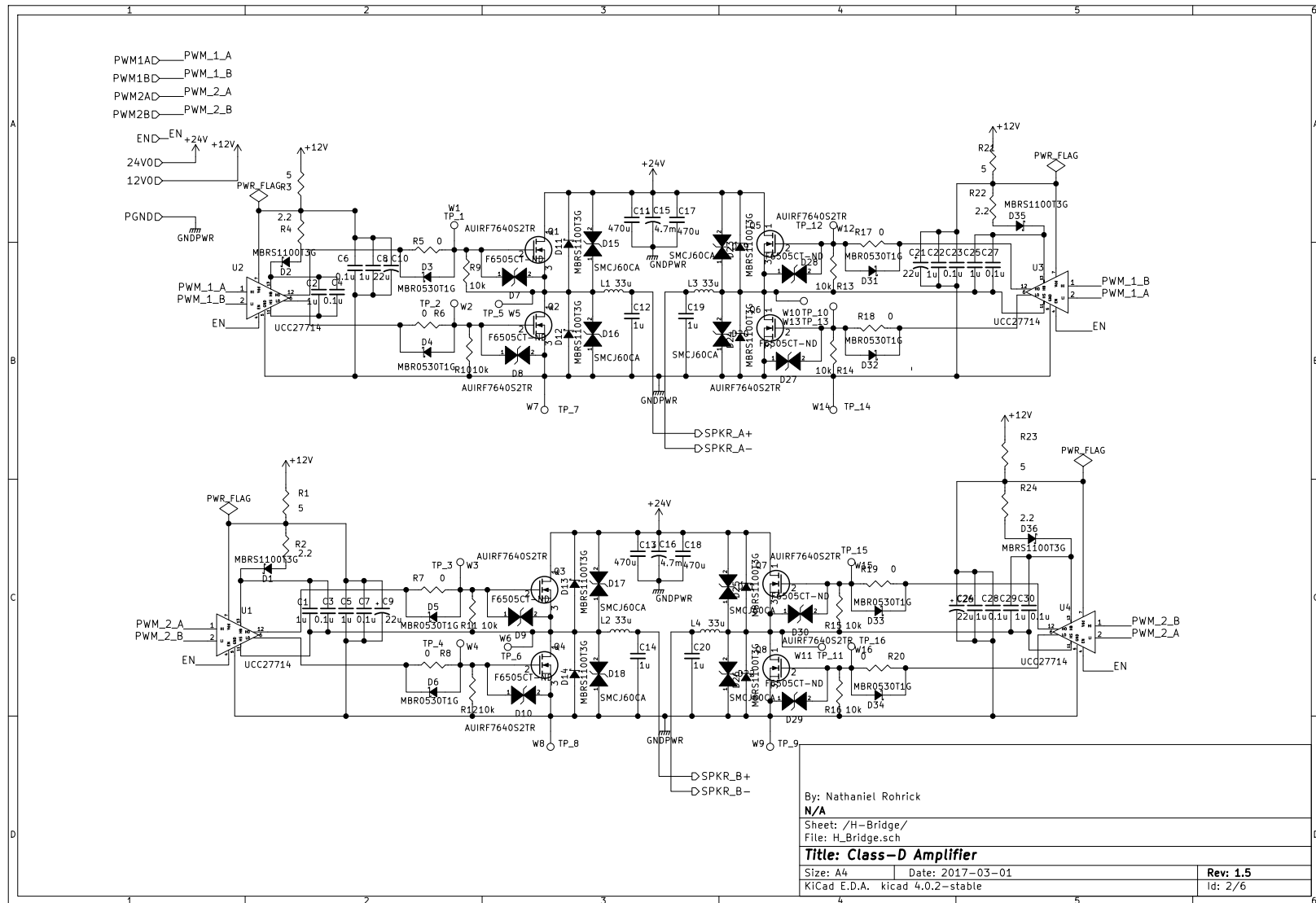


Figure 13: Class-D amplifier schematic pg. 5/6


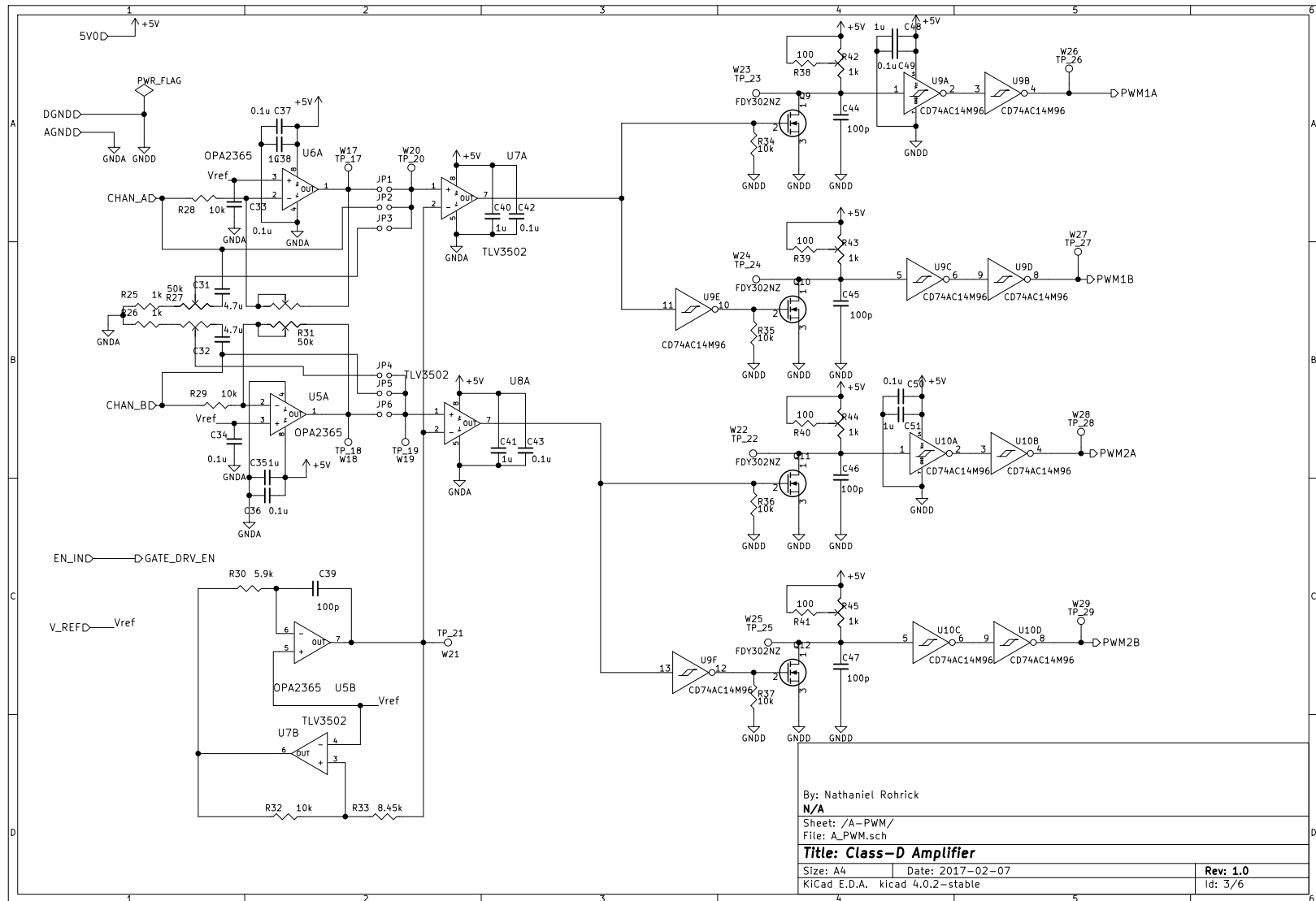


Figure 14: Class-D amplifier schematic pg. 3/6

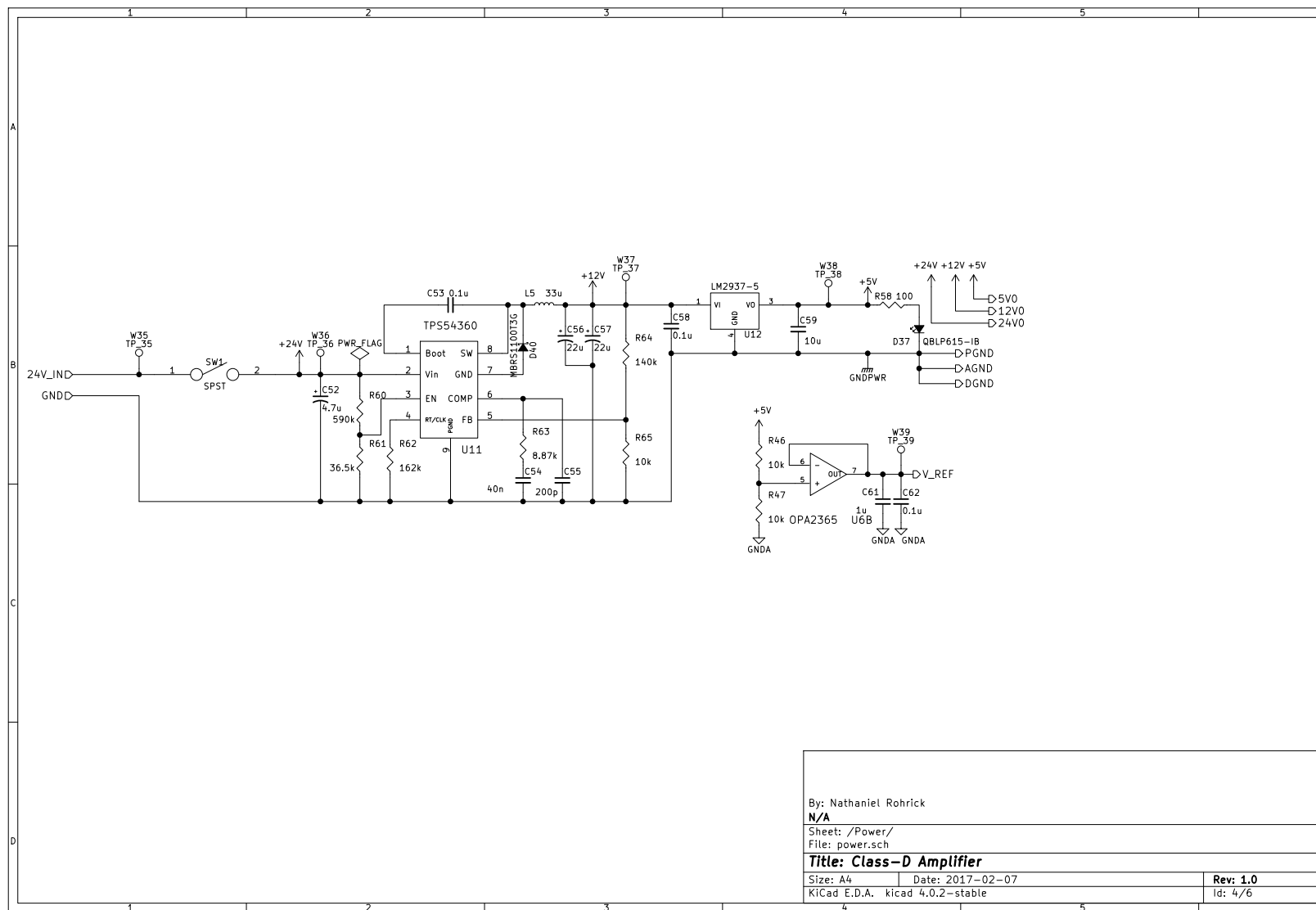

By: Nathaniel Rohrick
 N/A
 Sheet: /Power/
 File: power.sch
Title: Class-D Amplifier
 Size: A4 | Date: 2017-02-07 | Rev: 1.0
 KiCad E.D.A. kicad 4.0.2-stable | Id: 4/6

Figure 15: Class-D amplifier schematic pg. 4/6

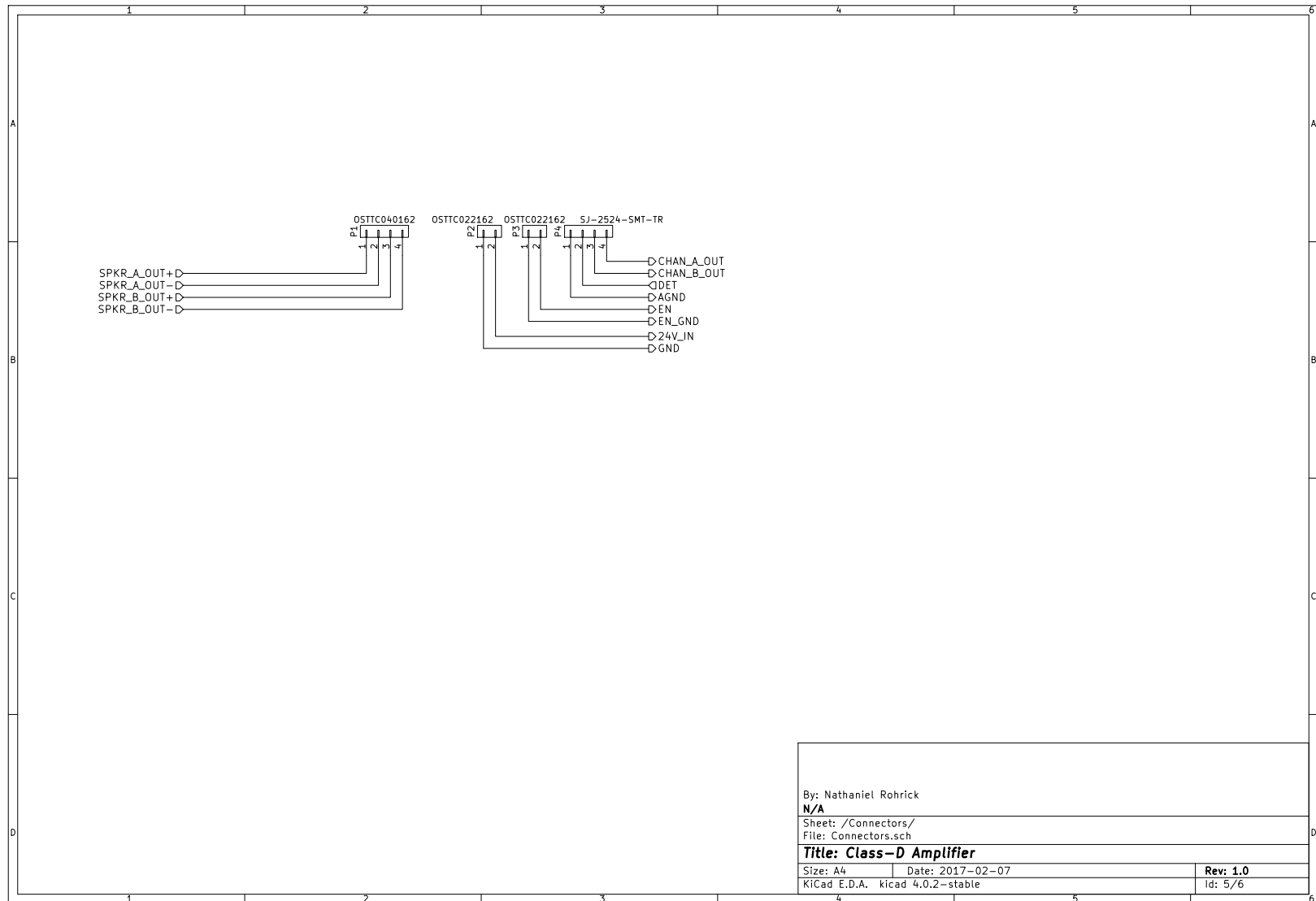


Figure 16: Class-D amplifier schematic pg. 5/6

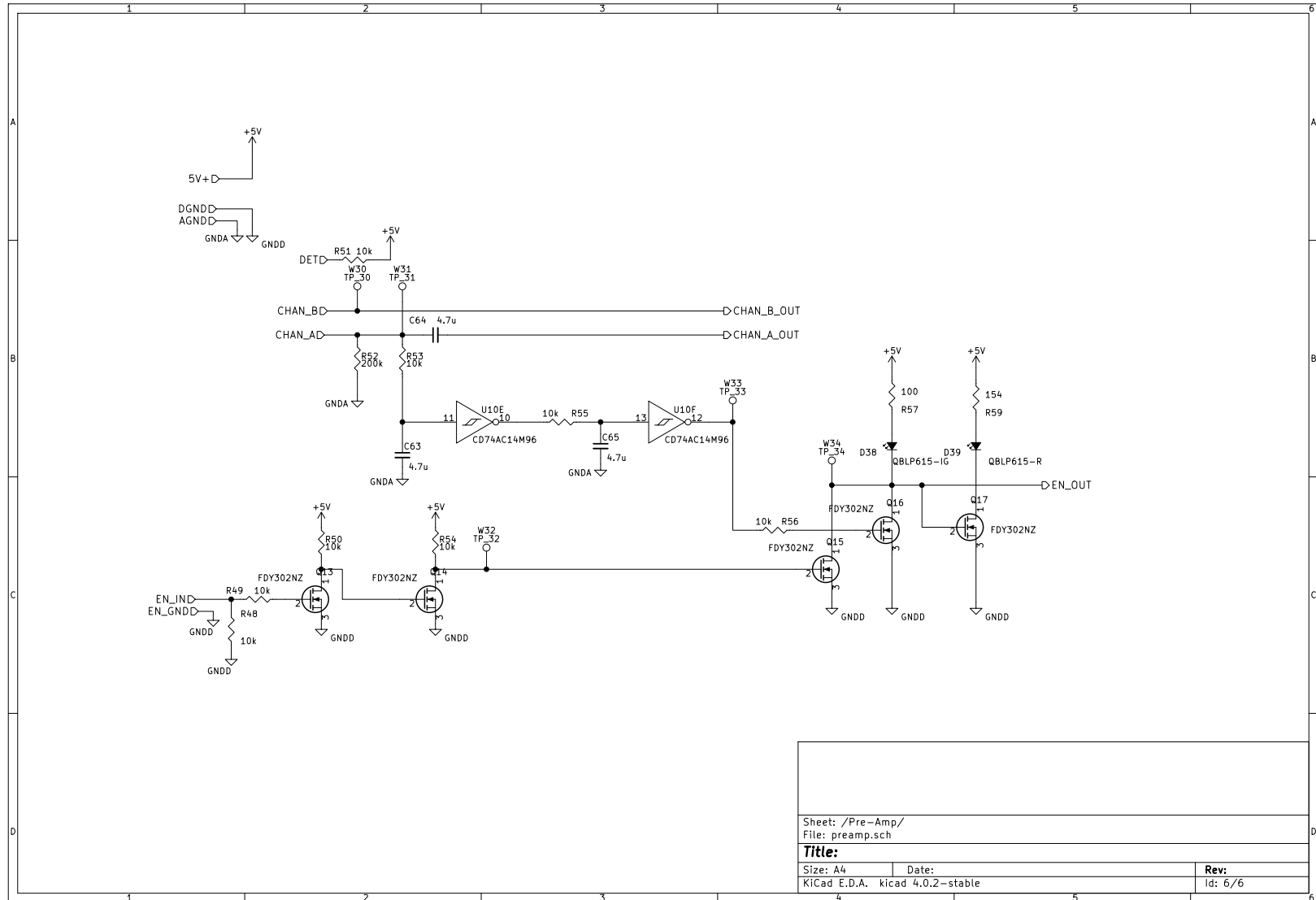


Figure 17: Class-D amplifier schematic pg. 6/6

6.3 Software Listings

Listing 1: musicplayer_top.sv

```
1 // Author: Preston Thompson & Nathaniel Rohrick
2 // Date: April 7, 2017
3
4 module musicplayer_top (
5     input logic CLOCK_50,
6     output logic [15:0] LED,
7     input logic [1:0] KEY,
8     input logic SDC_MISO,
9     output logic SDC_SCK,
10    output logic SDC_MOSI,
11    output logic SDC_N_SS,
12    output logic dac_dout,
13    output logic dac_lrcout,
14    output logic dac_sckout,
15    output logic dac_bckout,
16    (* altera_attribute = "-name WEAK_PULL_UP_RESISTOR ON" *)
17    input logic [3:0] keypad_kpr,
18    output logic [3:0] keypad_kpc
19 );
20
21    musicplayer u0 (
22        .clk_clk(CLOCK_50),
23        .reset_reset_n(KEY[0]),
24        .ledc_conn_leds(LED),
25        .sdc_conn_miso(SDC_MISO),
26        .sdc_conn_mosi(SDC_MOSI),
27        .sdc_conn_sck(SDC_SCK),
28        .sdc_conn_n_ss(SDC_N_SS),
29        .dac_conn_dout(dac_dout),
30        .dac_conn_lrcout(dac_lrcout),
31        .dac_conn_sckout(dac_sckout),
32        .dac_conn_bckout(dac_bckout),
33        .keypad_conn_kpc(keypad_kpc),
34        .keypad_conn_kpr(keypad_kpr)
35    );
36
37 endmodule
```

Listing 2: ledc.sv

```
1 // Author: Preston Thompson
2 // Date: April 7, 2017
3
4 module ledc (
5     input logic reset,
6     input logic clk,
7
8     input logic avs_read,
9     input logic avs_write,
10    input logic [15:0] avs_writedata,
```

```

11     output logic [15:0] avs_readdata,
12
13     output logic [15:0] leds
14 );
15
16     always_ff @(posedge clk) begin
17         if (reset) begin
18             leds <= '0;
19         end else begin
20             if (avs_write) begin
21                 leds <= avs_writedata;
22             end else if (avs_read) begin
23                 avs_readdata <= leds;
24             end
25         end
26     end
27
28 endmodule

```

Listing 3: dac.sv

```

1 // Author: Preston Thompson
2 // Date: April 7, 2017
3
4 module dac #(
5     // 50 MHz / (15625/7056) = 22.5792 MHz
6     parameter SCK_NUMERATOR = 16'd15625,
7     parameter SCK_DENOMINATOR = 16'd7056,
8     parameter BUFFER_SIZE = 2048
9 ) (
10     input logic reset,
11     input logic clk,
12
13     output logic dout,
14     output logic lrcout,
15     output logic sckout,
16     output logic bckout,
17
18     input logic avs_write,
19     input logic avs_read,
20     input logic [31:0] avs_writedata,
21     output logic [31:0] avs_readdata,
22     input logic [3:0] avs_address
23 );
24
25     logic [31:0] sample_buf[BUFFER_SIZE-1:0];
26     logic [10:0] sample_read_ptr;
27     logic [10:0] sample_write_ptr;
28
29     logic [15:0] sck_count;
30     logic [15:0] sck_count_next;
31     logic [2:0] bck_count;
32     logic [4:0] lrcout_count;
33     logic [31:0] sample;

```



```

34 logic [4:0] dout_ptr;
35 enum logic {increment, overflow} op;
36
37 always_ff @(posedge clk) begin
38
39     if (reset) begin
40
41         sck_count <= '0;
42         bck_count <= '0;
43         lrcout_count <= '0;
44         lrcout <= '1;
45         sckout <= '0;
46         bckout <= '0;
47         dout_ptr <= '0;
48         sample_write_ptr <= '0;
49         sample_read_ptr <= '0;
50
51     end else begin
52
53         // if the ring buffer is empty, output zeros and nop
54         if (sample_read_ptr != sample_write_ptr) begin
55             dout <= sample[5'hf - dout_ptr];
56             sck_count <= sck_count_next;
57         end else begin
58             dout <= '0;
59         end
60
61         // handle any reads from the CPU
62         if (avs_read) begin
63             unique case (avs_address)
64                 4'h0: begin
65                     avs_readdata[31:16] <= '0;
66                     avs_readdata[15:0] <= sample_read_ptr;
67                 end
68                 4'h1: begin
69                     avs_readdata[31:16] <= '0;
70                     avs_readdata[15:0] <= sample_write_ptr;
71                 end
72                 4'h2: begin
73                     avs_readdata <= sample_buf[sample_write_ptr];
74                 end
75             endcase
76         end
77
78         // handle any writes from the CPU
79         else if (avs_write) begin
80             unique case (avs_address)
81                 4'h0: begin
82                     sample_read_ptr <= avs_writedata[15:0];
83                 end
84                 4'h1: begin
85                     sample_write_ptr <= avs_writedata[15:0];
86                 end
87                 4'h2: begin

```

```

88         sample_buf[sample_write_ptr] <= avs_writedata;
89         sample_write_ptr <= sample_write_ptr + 16'd1;
90     end
91     endcase
92 end
93
94 // only interact with the DAC if there's samples in the ring buffer
95 if (op == overflow && sample_read_ptr != sample_write_ptr) begin
96     sckout <= ~sckout;
97     bck_count <= bck_count + 3'b1;
98     if (bck_count == '1) begin
99         lrcout_count <= lrcout_count + 5'b1;
100        bckout <= ~bckout;
101        if (bckout) begin
102            dout_ptr <= dout_ptr + 5'b1;
103        end
104        if (lrcout_count == '1) begin
105            lrcout <= ~lrcout;
106        end
107    end
108 end
109
110 if (dout_ptr == '1 &&
111     bck_count == '1 &&
112     op == overflow &&
113     lrcout_count == '1
114 ) begin
115     sample_read_ptr <= sample_read_ptr + 16'd1;
116     sample <= sample_buf[sample_read_ptr + 16'd1];
117 end
118
119 end
120 end
121
122 always_comb begin
123
124     if (sck_count >= (SCK_NUMERATOR - SCK_DENOMINATOR)) begin
125         sck_count_next = sck_count - (SCK_NUMERATOR - SCK_DENOMINATOR);
126         op = overflow;
127     end else begin
128         sck_count_next = sck_count + SCK_DENOMINATOR;
129         op = increment;
130     end
131
132 end
133
134 endmodule

```

Listing 4: dac_tb.sv

```

1 // Author: Preston Thompson
2 // Date: April 7, 2017
3
4 module dac_tb;

```

```

5
6   logic reset;
7   logic clk;
8
9   // HALF SCALE SINE
10  logic [15:0] lsamples [16] = '{
11      16'd0, 16'd6122, 16'd11313, 16'd14782,
12      16'd16000, 16'd14782, 16'd11313, 16'd6122,
13      16'd0, -16'd6122, -16'd11313, -16'd14782,
14      -16'd16000, -16'd14782, -16'd11313, -16'd6122
15  };
16  logic [15:0] rsamples [16] = '{
17      16'd0, 16'd6122, 16'd11313, 16'd14782,
18      16'd16000, 16'd14782, 16'd11313, 16'd6122,
19      16'd0, -16'd6122, -16'd11313, -16'd14782,
20      -16'd16000, -16'd14782, -16'd11313, -16'd6122
21  };
22
23  logic avs_write;
24  logic avs_read;
25  logic [31:0] avs_writedata;
26  logic [3:0] avs_address;
27
28  wire dout;
29  wire lrcout;
30  wire sckout;
31  wire bckout;
32  wire [31:0] avs_readdata;
33
34  dac dac_0(.*);
35
36  initial begin
37
38      // initial state
39      reset = 1;
40      clk = 0;
41      avs_write = 0;
42      avs_read = 0;
43
44      repeat (2) begin
45          #10ns; clk = ~clk;
46      end
47
48      reset = 0;
49
50      repeat (10) begin
51          #10ns; clk = ~clk;
52      end
53
54      avs_address = 4'h8;
55      avs_write = 1;
56      for (int i = 0; i < 16; i++) begin
57          avs_writedata = {lsamples[i], rsamples[i]};
58          repeat (2) begin

```

```

59         #10ns; clk = ~clk;
60     end
61 end
62
63     avs_write = 0;
64
65     repeat (64000) begin
66         #10ns; clk = ~clk;
67     end
68
69     $stop;
70
71 end
72
73 endmodule

```

Listing 5: spi.sv

```

1 //Author: Nathaniel Rohrick
2 //Date: April 7, 2017
3
4 module spi (
5     input logic clk,           //master clk
6     input logic reset,        //master reset
7     input logic miso,         //rx data from sd card
8
9     input logic avs_write,     //write flag from cpu
10    input logic avs_read,      //read flag from cpu
11    input logic [2:0] avs_address, //cpu address bus
12    input logic [31:0] avs_writedata, //cpu data output bus
13
14    output logic [31:0] avs_readdata, //cpu data input bus
15    output logic sck,          //sd card clock
16    output logic mosi,         //tx data to sd card
17    output logic n_ss          //chip select
18 );
19 //Below shows the memory allocation of the registers needed by spi.sv
20 /*
21 ADDRESS BEGIN | ADDRESS END | REG NAME | DESCRIPTION
22 -----
23 0x0000        | 0x0000    | data     | MOSI data buffer to be send out
24 0x0001        | 0x0001    | rcv_buf  | MISO buffer to recieve data
25 0x0002        | 0x0002    | div      | sck frequency divider register
26 0x0003        | 0x0003    | busy     | Tells spi caller if peripheral is busy
27 0x0004        | 0x0004    | n_ss     | peripheral enable
28 -----
29 */
30 localparam DATA_START = 8'h0;
31 localparam RCV_START = 8'h1;
32 localparam DIV_START = 8'h2;
33 localparam BUSY_START = 8'h3;
34 localparam SS_START = 8'h4;
35
36 //CPU visible registers

```

```

37 logic [7:0] data;           //data to send to slave
38 logic [7:0] rcv_buf;       //rcv buffer that holds data from send
39 logic [7:0] div;           //frequency divider register
40 logic busy;                //busy flag (1 when busy, 0 otherwise)
41 //End memory register description
42
43 localparam BYTE = 16'd8;   //size of a byte
44
45 enum {init, idle, snd_rcv} state, state_next;
46
47 logic [15:0] sck_freq_cnt;  //loaded with number of clk cycles
48 logic [15:0] sck_cnt;      //loaded with number of sck
49 logic [7:0] mosi_ptr;      //pointer to select cmd_buf bit
50 logic [7:0] miso_ptr;      //pointer to select cmd_buf byte
51 logic [7:0] divider;       //variable to make div the actual clock divider rate
52
53 assign divider = div >> 1'd1; //divide by 2 for usability on the firmware side
54
55 //state exit conditions
56 //allow data to latch on falling edge
57 assign SND_RCV_EXIT = ((sck_cnt == 16'd0)&&(sck == 0));
58 assign IDLE_EXIT = (avs_write && (avs_address == DATA_START));
59
60 always_ff @(posedge clk) begin
61     if (avs_read && (avs_address == BUSY_START)) begin
62         avs_readdata[0] <= busy;
63         avs_readdata[31:1] <= '0;
64     end
65
66     state <= state_next;
67
68     if (state_next == init)
69         busy <= 1;
70     else if (state_next == idle) begin
71         busy <= 0;
72         sck_cnt <= BYTE; //load with number of sck cycles
73         sck_freq_cnt <= divider; //load with number of clk cycles
74         mosi_ptr <= 8'h7; //get mosi_ptr looking at MSb of data
75         miso_ptr <= 8'h7; //get miso_ptr looking at MSb of rcv_buf
76         mosi <= 1'd1;
77         sck <= 1'd0;
78     end
79     else if (state_next == snd_rcv)
80         busy <= 1;
81
82     unique case (state)
83     init: begin
84         div <= 8'd1; //default clk divide is (2/2)*2 = 2
85         sck_cnt <= 16'd8; //load with number of sck cycles
86         sck_freq_cnt <= divider; //load with number of clk cycles
87         mosi_ptr <= 8'h7; //get mosi_ptr looking at MSb of data
88         miso_ptr <= 8'h7; //get miso_ptr looking at MSb of rcv_buf
89         rcv_buf <= 8'hFF; //default MISO state is high
90         data <= 8'hFF; //default data state is 0xFF

```

```

91     mosi <= 1'd1;           //default MOSI state is high
92     sck <= 1'd0;           //default sck state is high
93     n_ss <= 1'd1;          //de-select chip
94 end
95
96 idle: begin
97     //if CPU requests to read/write, allow to do so in idle
98     if (avs_write && (avs_address == DATA_START))
99         data <= avs_writedata[7:0];
100
101     if (avs_read && (avs_address == RCV_START)) begin
102         avs_readdata[31:8] <= 24'd0;
103         avs_readdata[7:0] <= rcv_buf;
104     end else if (avs_read && (avs_address == DIV_START)) begin
105         avs_readdata[31:8] <= 24'd0;
106         avs_readdata[7:0] <= div;
107     end
108
109     if (avs_write && (avs_address == DIV_START))
110         div <= avs_writedata[7:0];
111
112     if (avs_write && (avs_address == SS_START))
113         n_ss <= avs_writedata[0];
114
115 end
116
117 snd_rcv: begin
118
119     if (sck_freq_cnt == 16'd0) begin
120         sck_freq_cnt <= divider;
121         sck <= ~sck;
122     end else begin
123         sck_freq_cnt <= sck_freq_cnt - 16'd1;
124     end
125
126     if ((sck == 1'd0) && (sck_freq_cnt == 16'd0)) begin //latch on rising edge
127         sck_cnt <= sck_cnt - 16'd1;
128         rcv_buf[miso_ptr] <= miso;
129         miso_ptr <= miso_ptr - 8'd1;
130         mosi_ptr <= mosi_ptr - 8'd1;
131     end
132
133     if (sck && (sck_freq_cnt == 16'd0)) begin //shift on falling egde
134         mosi <= data[mosi_ptr];
135         //put valid data on mosi (spi mode 0)
136     end else if ((sck_cnt == 16'd8) && (sck_freq_cnt == divider)) begin
137         mosi <= data[mosi_ptr];
138     end
139 end
140
141 endcase
142 end
143
144 //bring system to next state

```

```

145 always_comb begin
146     case (state)
147     init: begin
148         if (reset)
149             state_next <= init;
150         else
151             state_next <= idle;
152     end
153
154     idle: begin
155         if (reset)
156             state_next <= init;
157         else if (IDLE_EXIT)
158             state_next <= snd_rcv;
159         else
160             state_next <= idle;
161     end
162
163     snd_rcv: begin
164         if (reset)
165             state_next <= init;
166         else if (SND_RCV_EXIT)
167             state_next = idle;
168         else
169             state_next = snd_rcv;
170
171     end
172 endcase
173 end
174 endmodule

```

Listing 6: spi_tb.sv

```

1 // Author: Preston Thompson
2 // Date: April 7, 2017
3
4 module spi_tb();
5
6     logic clk;
7     logic reset;
8
9     logic avs_write;
10    logic avs_read;
11    logic [2:0] avs_address;
12    logic [31:0] avs_writedata;
13
14    wire [31:0] avs_readdata;
15    wire sck;
16    wire mosi;
17    wire n_ss;
18
19    spi DUT(.*);
20
21    assign miso = mosi;

```

```

22
23     initial begin
24
25         // initial state
26         reset = 1;
27         clk = 0;
28         avs_write = 0;
29         avs_read = 0;
30
31         // perform a reset
32         repeat(2) begin
33             #10ns; clk = ~clk;
34         end
35
36         reset = 0;
37
38         // idle for a bit
39         repeat (10) begin
40             #10ns; clk = ~clk;
41         end
42
43         // write to baud div register
44         avs_address = 3'h2;
45         avs_write = 1;
46         avs_writedata = 32'd4;
47         repeat (2) begin
48             #10ns; clk = ~clk;
49         end
50         avs_write = 0;
51
52         // idle for a bit
53         repeat (10) begin
54             #10ns; clk = ~clk;
55         end
56
57         // deassert ss
58         avs_address = 3'h4;
59         avs_write = 1;
60         avs_writedata = 32'd1;
61         repeat (2) begin
62             #10ns; clk = ~clk;
63         end
64         avs_write = 0;
65
66         // idle for a bit
67         repeat (10) begin
68             #10ns; clk = ~clk;
69         end
70
71         // assert ss
72         avs_address = 3'h4;
73         avs_write = 1;
74         avs_writedata = 32'd0;
75         repeat (2) begin

```



```

76         #10ns; clk = ~clk;
77     end
78     avs_write = 0;
79
80     // idle for a bit
81     repeat (10) begin
82         #10ns; clk = ~clk;
83     end
84
85     // write a byte
86     avs_address = 3'h0;
87     avs_write = 1;
88     avs_writedata = 32'ha5;
89     repeat (2) begin
90         #10ns; clk = ~clk;
91     end
92     avs_write = 0;
93
94     // many cycles
95     repeat (100) begin
96         #10ns; clk = ~clk;
97     end
98
99     // read the busy bit
100    avs_address = 3'h3;
101    avs_read = 1;
102    repeat (2) begin
103        #10ns; clk = ~clk;
104    end
105    avs_read = 0;
106
107    // idle for a bit
108    repeat (10) begin
109        #10ns; clk = ~clk;
110    end
111
112    end
113
114 endmodule

```

Listing 7: sdc.c

```

1 //Author: Nathaniel Rohrick
2 //Date: April 7, 2017
3
4 #include "../musicplayer_bsp/system.h"
5 #include <stdbool.h>
6 #include <stdint.h>
7 #include "sdc_cmd.h"
8 #include "sdc.h"
9
10
11 static volatile const uint8_t* const spi_sdc =
12     (volatile uint8_t*)SDC_SPI_0_BASE;

```

```

13 static volatile uint8_t* const spi_data =
14     (volatile uint8_t*)(SDC_SPI_0_BASE + 0x00);
15 static volatile uint8_t* const spi_rcvBuf =
16     (volatile uint8_t*)(SDC_SPI_0_BASE + 0x04);
17 static volatile uint8_t* const spi_div =
18     (volatile uint8_t*)(SDC_SPI_0_BASE + 0x08);
19 static volatile uint8_t* const spi_n_ready =
20     (volatile uint8_t*)(SDC_SPI_0_BASE + 0x0C);
21 static volatile uint8_t* const spi_n_ss =
22     (volatile uint8_t*)(SDC_SPI_0_BASE + 0x10);
23 static volatile uint8_t * const ledc =
24     (volatile uint8_t *)LEDC_0_BASE;
25
26 static const uint32_t WORD_LEN = 32;
27 static const uint8_t STARTb = 0x40;
28
29 static const uint8_t dByte = 0xff;    //dummy byte, all 1's
30 static const uint8_t idleb = 0x01;    //idle bit
31 static const uint8_t respb = 0xFE;    //response good byte
32 static const uint32_t CLK = 50000000; //clk rate of fpga
33
34 //Function: sdInit
35 //Arguments: None
36 //Return: true when error
37 //Description: Initializes an spi communications interface with an external
38 //sd card. Puts sd card into spi mode and sets clock divider to default 2.
39 bool sdc_init ()
40 {
41     uint8_t resp_buf[5];
42
43     for (int i = 0; i < 50000; i++); //delay 1ms
44
45     if (baud_set(126)) //set sck to 50M/126~=400kHz
46         return true;
47
48     while (*spi_n_ready);
49     *spi_n_ss = 1; //deassert SS
50     for (int i = 0; i < 50000; i++); //delay 1ms
51     for (int i = 0; i < 200; i++)
52     {
53         while (*spi_n_ready);
54         *spi_data = dByte;
55     }
56
57     for (int i = 0; i < 50000; i++); //delay 1ms
58
59     if (sdc_send_cmd(CMD0, 0x0, R1, resp_buf)) //send CMD0
60         return true;
61
62     if (sdc_send_cmd(CMD8, 0x1AA, R7, resp_buf))
63         return true;
64
65     while (*spi_n_ready);
66

```

```

67     if (*resp_buf > 1)
68         return true;
69
70     for (int i = 0; i <= TIMEOUT; i++)
71     {
72         if (sdc_send_cmd(CMD55, 0x0, R1, resp_buf))
73             return true;
74
75         while (*spi_n_ready);
76
77         if (*resp_buf > 1)
78             continue;
79
80         if (sdc_send_cmd(CMD41, 0x40000000, R1, resp_buf))
81             return true;
82
83         if (*resp_buf > 0)
84             continue;
85         else
86             break;
87     }
88     sdc_send_cmd(CMD16, BLOCK_SIZE, R1, resp_buf);
89     while (*spi_n_ready);
90     if (*resp_buf > 0)
91         return true;
92     return(baud_set(2));
93 }
94
95 //Function: baud_set
96 //Arguments: uint8 div divides clk by a value between 2 and 255
97 //Return: True wiith error
98 //Description: Sets clk divider to generate sck, the spi clock
99 bool baud_set (uint8_t div)
100 {
101     while (*spi_n_ready);
102     *spi_div = div;
103     return false;
104 }
105 //Function: sdc_send_cmd
106 //Arguments: takes a command number and a corresponding payload
107 // and an expected response type in resp. It loads the response
108 // into resp_buf.
109 //Return: True when error
110 //Description: Sends a command to SD card and loads a buffer with
111 // the response.
112 bool sdc_send_cmd(
113     const uint8_t cmd,
114     const uint32_t payload,
115     const uint8_t resp,
116     uint8_t* resp_buf
117 )
118 {
119     uint16_t spi_timeout;
120     while (*spi_n_ready);

```

```

121 *spi_n_ss = 0; // assert SS
122 while (*spi_n_ready);
123 *spi_data = dByte;
124 //send cmd index
125 while (*spi_n_ready);
126 *spi_data = cmd | STARTb;
127
128 //send payload MSB first
129 for (int i = 3; i >= 0; i--)
130 {
131     while (*spi_n_ready);
132     *spi_data = (payload >> (i*8));
133 }
134
135 //send CRC
136 while (*spi_n_ready);
137 if (resp == R1 || resp == R1b)
138     *spi_data = DEF_CRC;
139 else if (resp == R7)
140     *spi_data = CMD8_CRC;
141
142 while (*spi_n_ready);
143 *spi_data = dByte;
144
145 for (spi_timeout = 0; spi_timeout < TIMEOUT; spi_timeout++)
146 {
147     while (*spi_n_ready);
148     if (*spi_rcvBuf & (1 << 7))
149         *spi_data = dByte; //send another byte
150     else if (resp == R1)
151     {
152         *resp_buf = *spi_rcvBuf;
153         break;
154     }
155     else if (resp == R7)
156     {
157         while (*spi_n_ready);
158         *resp_buf = *spi_rcvBuf;
159         for (int i = 1; i < 5; i++)
160         {
161             while (*spi_n_ready);
162             *spi_data = dByte;
163             *(resp_buf + i) = *spi_rcvBuf;
164         }
165         break;
166     }
167     else if (resp == R1b)
168     {
169         do
170         {
171             while (*spi_n_ready);
172             *spi_data = dByte;
173             while (*spi_n_ready);
174         }

```

```

175     while(*spi_rcvBuf != 0xFF);
176     break;
177 }
178 }
179
180 if (((cmd == CMD17 )||(cmd == CMD18))&&(spi_timeout != TIMEOUT))
181     return false;
182
183 while (*spi_n_ready);
184 *spi_n_ss = 1;//deassert SS
185
186
187 //if (spi_timeout == TIMEOUT)
188     //return true;
189
190     while (*spi_n_ready);
191     *spi_data = dByte;
192     while (*spi_n_ready);
193     *spi_data = dByte;
194
195     return false;
196 }
197
198 bool sdc_read(
199     uint32_t addr,
200     uint8_t len,
201     uint8_t* buf
202 )
203 {
204     uint8_t resp_buf[8];
205     if (sdc_send_cmd(CMD18, addr, R1, resp_buf))
206         return true;
207
208     //if (resp_buf[0] != 0)
209         //return true;
210
211     while (*spi_n_ready);
212     *spi_data = dByte;
213
214     for (int iblock = 0; iblock < len; iblock++)
215     {
216         for (int i = 0; i <= TIMEOUT; i++)
217         {
218             while (*spi_n_ready);
219             if (*spi_rcvBuf == 0xFE)
220                 break;
221             else
222             {
223                 while (*spi_n_ready);
224                 *spi_data = dByte;
225             }
226             //if (i == TIMEOUT)
227                 //return true;
228         }

```

```

229
230
231 //unsigned block_offs = iblock * BLOCK_SIZE;
232 uint8_t *end = buf + BLOCK_SIZE;
233 for (; buf < end; buf++)//work starts here
234 {
235     while (*spi_n_ready);
236     *spi_data = dByte;
237     while (*spi_n_ready);
238     *buf = *spi_rcvBuf;
239     //buf[i + block_offs] = *spi_rcvBuf;
240     // *buf++ = *spi_rcvBuf;
241 }
242 }
243 while (*spi_n_ready);
244 *spi_data = dByte;
245 while (*spi_n_ready);
246 *spi_data = dByte;
247
248 if (sdc_send_cmd(CMD12, 0x0, R1b, resp_buf)) //stop transmission
249     return true;
250
251 //if (resp_buf[0] != 0)
252 //return true;
253
254 //while (*spi_n_ready);
255 // *spi_n_ss = 1;//deassert SS
256 return false;
257 }

```

Listing 8: sdc.h

```

1 // Author: Nathaniel Rohrick
2 // Date: April 7, 2017
3
4 #ifndef _SDC_H
5 #define _SDC_H
6
7 #include <stdbool.h>
8 #include "system.h"
9
10 bool baud_set (uint8_t div);
11 bool sdc_init ();
12 bool sdc_read(uint32_t addr, uint8_t len, uint8_t* buf);
13 bool sdc_send_cmd(const uint8_t cmd, const uint32_t payload,
14     const uint8_t resp, uint8_t* const resp_buf);
15 #define BLOCK_SIZE 512
16
17 #endif

```

Listing 9: sdc_cmd.h

```

1 // Author: Nathaniel Rohrick
2 // Date: April 7, 2017

```

```

3
4 /*
5 Command breakdown
6 -----
7 B1      | B1 - B5 | B6
8 -----
9 index | payload | CRC
10 -----
11 */
12 //name and payload for commands, use 0x95 for CRC (not used)
13
14 #define CMD0  0
15 #define CMD1  1
16 #define CMD8  8
17 #define CMD9  9
18 #define CMD10 10
19 #define CMD12 12
20 #define CMD16 16
21 #define CMD17 17
22 #define CMD18 18
23 #define CMD23 23
24 #define CMD24 24
25 #define CMD25 25
26 #define CMD41 41
27 #define CMD55 55
28 #define CMD58 58
29
30 #define DEF_CRC 0x95
31 #define CMD8_CRC 0x87
32
33 #define R1 1
34 #define R7 2
35 #define R1b 3
36
37 #define TIMEOUT 100000

```

Listing 10: keypad.sv

```

1 //Author Nathaniel Rohrick
2 //Date: April 7, 2017
3
4 module keypad(
5     input logic [3:0] kpr,           //row vector on keypad
6     input logic reset,             //master reset
7     input logic clk,               //master clk
8
9     input logic avs_write,         //write flag from cpu
10    input logic avs_read,          //read flag from cpu
11    input logic [1:0] avs_address,  //cpu address bus
12    input logic [31:0] avs_writedata, //cpu data output bus
13
14    output logic [31:0] avs_readdata, //cpu data input bus
15    output logic [3:0] kpc          //column vector on keypad
16 );

```

```

17
18 //localparam KPHIT_START = 3'd0; //start address for keypad hit flag
19 localparam BUTTON_START = 1'd0; //start address for decoded keypress register
20
21 localparam WAIT = 22'h3FFFFFF; //~~100ms delay for debouncing
22     localparam DIV = 16'd62500; //clk divider for polling CLK/(4*DIV)
23
24 logic kphit; //high when keypad is pressed
25     logic [3:0] kpr_reg;
26 logic [21:0] dbnc_cnt; //debounce counter
27 logic [15:0] clk_cnt; //clk frequency counter
28
29 enum {blank, next, v_up, v_down, mute, prev} button; //button state
30 enum {idle, active, rst} state, state_next; //state machine variables
31
32 //exit conditions
33 assign IDLE_EXIT = kphit;
34 assign ACTIVE_EXIT = !kphit && (dbnc_cnt == '0);
35
36 //datapath
37 always_ff@(posedge clk) begin
38     state <= state_next;
39     kpr_reg <= kpr;
40
41     if (clk_cnt == '0)
42         clk_cnt <= DIV;
43     else
44         clk_cnt <= clk_cnt - 'd1;
45
46 //always handle requests for keypress info
47 if (avs_read && (avs_address == BUTTON_START)) begin
48     avs_readdata[31:3] <= '0;
49     avs_readdata[2:0] <= button;
50 end
51
52 case (state)
53     rst: begin //load default states
54         kpc <= 4'b0111;
55         dbnc_cnt <= WAIT;
56     end
57
58     idle: begin
59         dbnc_cnt <= WAIT; //prep debounce counter
60         if (state_next == idle) begin //if key is pressed, only 1 to decode
61             if ((kpr_reg == 4'b1111) && (clk_cnt == 0)) begin
62                 unique case (kpc)
63                     4'b0111: kpc <= 4'b1011;
64                     4'b1011: kpc <= 4'b1101;
65                     4'b1101: kpc <= 4'b1110;
66                     4'b1110: kpc <= 4'b0111;
67                 endcase
68             end
69             if ((kpr_reg == 4'b1110) && (kpc == 4'b1110)) begin
70                 button <= blank;

```



```

71         kphit <= '1;
72     end else if ((kpr_reg == 4'b1110) && (kpc == 4'b1101)) begin
73         button <= blank;
74         kphit <= '1;
75     end else if ((kpr_reg == 4'b1110) && (kpc == 4'b1011)) begin
76         button <= blank;
77         kphit <= '1;
78     end else if ((kpr_reg == 4'b1110) && (kpc == 4'b0111)) begin
79         button <= blank;
80         kphit <= '1;
81     end else if ((kpr_reg == 4'b1101) && (kpc == 4'b1110)) begin
82         button <= blank;
83         kphit <= '1;
84     end else if ((kpr_reg == 4'b1101) && (kpc == 4'b1101)) begin
85         button <= blank;
86         kphit <= '1;
87     end else if ((kpr_reg == 4'b1101) && (kpc == 4'b1011)) begin
88         button <= v_down;
89         kphit <= '1;
90     end else if ((kpr_reg == 4'b1101) && (kpc == 4'b0111)) begin
91         button <= blank;
92         kphit <= '1;
93     end else if ((kpr_reg == 4'b1011) && (kpc == 4'b1110)) begin
94         button <= blank;
95         kphit <= '1;
96     end else if ((kpr_reg == 4'b1011) && (kpc == 4'b1101)) begin
97         button <= next;
98         kphit <= '1;
99     end else if ((kpr_reg == 4'b1011) && (kpc == 4'b1011)) begin
100        button <= blank;
101        kphit <= '1;
102    end else if ((kpr_reg == 4'b1011) && (kpc == 4'b0111)) begin
103        button <= prev;
104        kphit <= '1;
105    end else if ((kpr_reg == 4'b0111) && (kpc == 4'b1110)) begin
106        button <= blank;
107        kphit <= '1;
108    end else if ((kpr_reg == 4'b0111) && (kpc == 4'b1101)) begin
109        button <= blank;
110        kphit <= '1;
111    end else if ((kpr_reg == 4'b0111) && (kpc == 4'b1011)) begin
112        button <= v_up;
113        kphit <= '1;
114    end else if ((kpr_reg == 4'b0111) && (kpc == 4'b0111)) begin
115        button <= blank;
116        kphit <= '1;
117    end else begin
118        kphit <= 0;
119        button <= blank;
120    end
121 end
122 end
123
124 active: begin

```

```

125         dbnc_cnt <= dbnc_cnt - 'd1; //counts down
126             if (kpr_reg == 4'b1111)
127                 kphit <= 0;
128     end
129 endcase
130
131 end
132 //control path
133 always_comb begin
134     case(state)
135         rst: begin
136             if (reset)
137                 state_next = rst;
138             else
139                 state_next = idle;
140         end
141
142         idle: begin
143             if (reset)
144                 state_next = rst;
145             else if (IDLE_EXIT)
146                 state_next = active;
147             else
148                 state_next = idle;
149         end
150
151         active: begin
152             if (reset)
153                 state_next = rst;
154             else if (ACTIVE_EXIT)
155                 state_next = idle;
156             else
157                 state_next = active;
158         end
159     endcase
160 end
161 endmodule

```

Listing 11: keypad.c

```

1 // Author: Nathaniel Rohrick
2 // Date: April 7, 2017
3
4 #include <stdint.h>
5
6 #include "../musicplayer_bsp/system.h" //defines mapping memory of project
7 #include "keypad.h"
8
9 static volatile uint32_t * const keypad_button =
10     (volatile uint32_t *) (KEYPAD_0_BASE);
11
12 int keypad_get_button(void)
13 {
14     return *keypad_button;

```

15 }

Listing 12: keypad.h

```
1 // Author: Nathaniel Rohrick
2 // Date: April 7, 2017
3
4 #ifndef _KEYPAD_H
5 #define _KEYPAD_H
6
7 enum Keypad_Buttons {
8     key_blank,
9     key_next,
10    key_v_up,
11    key_v_down,
12    key_mute,
13    key_prev
14 };
15
16 int keypad_get_button(void);
17
18 #endif
```

Listing 13: main.c

```
1 // Author: Preston Thompson
2 // Date: April 7, 2017
3
4 #include <stdint.h>
5
6 #include "system.h"
7 #include "sdc.h"
8 #include "sdc_cmd.h"
9 #include "keypad.h"
10
11 #define DAC_BUFFER_SIZE 2048
12
13 static volatile uint16_t * const ledc =
14     (volatile uint16_t *)LEDC_0_BASE;
15 static volatile uint32_t * const dac_sample_read_ptr =
16     (volatile uint32_t *)DAC_0_BASE;
17 static volatile uint32_t * const dac_sample_write_ptr =
18     (volatile uint32_t *) (DAC_0_BASE + 0x4);
19 static volatile uint32_t * const dac_sample =
20     (volatile uint32_t *) (DAC_0_BASE + 0x8);
21
22 struct track_info {
23     uint32_t start;
24     uint32_t size;
25 };
26
27 static struct track_info tracks[64];
28 static uint8_t buf[512];
29 static int current_track;
```

```

30 static uint32_t current_sector;
31 static uint32_t last_sector;
32 static int num_tracks;
33
34 int get_num_samples(void) {
35     volatile uint32_t write_ptr = *dac_sample_write_ptr;
36     volatile uint32_t read_ptr = *dac_sample_read_ptr;
37     if (write_ptr >= read_ptr)
38         return write_ptr - read_ptr;
39     else
40         return (DAC_BUFFER_SIZE - read_ptr) + write_ptr;
41 }
42
43 void change_track(void) {
44     *ledc = current_track;
45     current_sector = tracks[current_track].start;
46     if (current_track != num_tracks - 1)
47         last_sector = tracks[current_track+1].start - 1;
48     else
49         last_sector = tracks[current_track].start + tracks[current_track].size/512;
50     sdc_read(current_sector, 1, buf);
51     while (keypad_get_button() != key_blank);
52 }
53
54 int main(void) {
55     int i;
56
57     *ledc = 0xff;
58
59     sdc_init();
60
61     sdc_read(0, 1, (uint8_t *)tracks);
62
63     current_track = 0;
64
65     for (i = 0; i < 64; i++) {
66         if (tracks[i].size > 0)
67             num_tracks++;
68     }
69
70     change_track();
71
72     while (1) {
73         int current_key = keypad_get_button();
74         if (current_key == key_next) {
75             current_track++;
76             if (current_track == num_tracks)
77                 current_track = 0;
78             change_track();
79             continue;
80         }
81         else if (current_key == key_prev) {
82             current_track--;
83             if (current_track < 0)

```

```

84         current_track = num_tracks - 1;
85         change_track();
86         continue;
87     }
88     else if (current_sector == last_sector) {
89         int dac_room = DAC_BUFFER_SIZE - get_num_samples();
90         if (dac_room >= (tracks[current_track].size % 512)/4) {
91             for (i = 0; i < tracks[current_track].size % 512; i+= 4)
92                 *dac_sample = *(uint32_t *)(buf + i);
93             if (current_track == num_tracks - 1)
94                 current_track = 0;
95             else
96                 current_track++;
97             change_track();
98             sdc_read(current_sector, 1, buf);
99         }
100     }
101     else {
102         int dac_room = DAC_BUFFER_SIZE - get_num_samples();
103         if (dac_room >= 128) {
104             for (i = 0; i < 512; i += 4)
105                 *dac_sample = *(uint32_t *)(buf + i);
106             current_sector++;
107             sdc_read(current_sector, 1, buf);
108         }
109     }
110 }
111
112     return 0;
113 }

```

Listing 14: fat.c

```

1 // Author: Preston Thompson
2 // Date: April 7, 2017
3
4 // This is an incomplete FAT32 driver.
5
6 #include <stddef.h>
7 #include <stdint.h>
8
9 #include "fat.h"
10 #include "sdc.h"
11
12 struct Partition_Desc {
13     uint8_t type_code;
14     uint32_t lba_begin;
15 };
16
17 struct Volume_ID {
18     uint16_t BytsPerSec;
19     uint8_t SecPerClus;
20     uint16_t RsvdSecCnt;
21     uint8_t NumFATs;

```

```

22     uint32_t FATSz32;
23     uint32_t RootClus;
24 };
25
26 static uint8_t sector_buf[512];
27 static struct Partition_Desc pd;
28 static struct Volume_ID vid;
29 static uint32_t cluster_begin_lba;
30 static uint32_t fat_begin_lba;
31
32 static void read_word(const uint8_t *src, void *dst, size_t len) {
33     size_t i;
34     for (i = 0; i < len; i++)
35         *(uint8_t*)(dst++) = *src++;
36 }
37
38 void fat_init(void) {
39     sdc_read(0, 1, sector_buf);
40     read_word(sector_buf + 446 + 0x04, &pd.type_code, 1);
41     read_word(sector_buf + 446 + 0x08, &pd.lba_begin, 4);
42     sdc_read(pd.lba_begin, 1, sector_buf);
43     read_word(sector_buf + 0x0b, &vid.BytsPerSec, 2);
44     read_word(sector_buf + 0x0d, &vid.SecPerClus, 1);
45     read_word(sector_buf + 0x0e, &vid.RsvdSecCnt, 2);
46     read_word(sector_buf + 0x10, &vid.NumFATs, 1);
47     read_word(sector_buf + 0x24, &vid.FATSz32, 4);
48     read_word(sector_buf + 0x2c, &vid.RootClus, 4);
49     fat_begin_lba = pd.lba_begin + vid.RsvdSecCnt;
50     cluster_begin_lba = fat_begin_lba + (vid.NumFATs * vid.FATSz32);
51 }
52
53 int fat_get_file_info(uint32_t index, struct File_Info *fi) {
54     uint8_t record[32];
55     uint16_t first_cluster_hi, first_cluster_lo;
56     uint32_t lba_addr;
57
58     lba_addr = cluster_begin_lba + (index / (vid.BytsPerSec / 32));
59
60     sdc_read(lba_addr, 1, sector_buf);
61
62     read_word(sector_buf + index * 32, record, 32);
63
64     if (record[0] == 0)
65         return FAT_END_OF_FILES;
66
67     if ((record[0x0b] & 0xF) == 0xF)
68         return FAT_LONG_FILENAME;
69
70     read_word(record, &fi->name, 11);
71     fi->name[11] = '\0';
72
73     fi->is_dir = (record[11] & (1 << 4)) ? 1 : 0;
74
75     read_word(record + 0x1a, &first_cluster_lo, 2);

```

```

76     read_word(record + 0x14, &first_cluster_hi, 2);
77     fi->first_cluster = first_cluster_lo | (first_cluster_hi << 16);
78
79     read_word(record + 0x1c, &fi->size, 4);
80
81     return FAT_SUCCESS;
82 }
83
84 static uint32_t lba_addr_from_cluster(uint32_t cluster) {
85     return (cluster - vid.RootClus) * vid.SecPerClus + cluster_begin_lba;
86 }
87
88 size_t fat_read_file(uint32_t index, uint32_t sector, uint8_t *dst) {
89     uint32_t lba_addr, cluster_num, cluster, i;
90     struct File_Info fi;
91
92     if (fat_get_file_info(index, &fi) != FAT_SUCCESS)
93         return 0;
94
95     cluster_num = sector / vid.SecPerClus;
96     cluster = fi.first_cluster;
97
98     for (i = 0; i < cluster_num; i++) {
99         sdc_read(fat_begin_lba + (cluster >> 7), 1, sector_buf);
100        read_word(sector_buf + (cluster & 0x7f) * 4, &cluster, 4);
101        if (cluster >= 0xFFFFFFFF)
102            return 0;
103    }
104
105    lba_addr = lba_addr_from_cluster(cluster) + (sector % vid.SecPerClus);
106
107    sdc_read(lba_addr, 1, dst);
108
109    read_word(sector_buf + (cluster & 0x7f) * 4, &cluster, 4);
110
111    if (cluster >= 0xFFFFFFFF)
112        return fi.size % BLOCK_SIZE;
113    else
114        return BLOCK_SIZE;
115 }

```

Listing 15: fat.h

```

1 // Author: Preston Thompson
2 // Date: April 7, 2017
3
4 #ifndef _FAT_H
5 #define _FAT_H
6
7 #include <stdint.h>
8 #include <stddef.h>
9
10 #define FAT_SUCCESS 0
11 #define FAT_END_OF_FILES 1

```

```

12 #define FAT_LONG_FILENAME 2
13
14 struct File_Info {
15     char name[12];
16     uint8_t is_dir;
17     uint32_t first_cluster;
18     uint32_t size;
19 };
20
21 void fat_init(void);
22 int fat_get_file_info(uint32_t index, struct File_Info *fi);
23 size_t fat_read_file(uint32_t index, uint32_t sector, uint8_t *dst);
24
25 #endif

```

Listing 16: deadtime.m

```

1 clc;
2 clear;
3 fp = fopen('deadtime.txt', 'w');
4 s = tf('s');
5
6 R_low = 100;      %Minimum resistor value (pot = 0)
7 R_high = 1000;
8
9 C = 100e-12;    %Capacitance value
10
11 H = (1/(R_low*C))/(s+(1/(R_low*C)));%Filter transfer function
12
13
14
15 %step(H);
16 S_min = stepinfo(H,'RiseTimeLimits',[0.00,0.52]);
17 S_max = stepinfo(H,'RiseTimeLimits',[0.00,0.68]);
18 S_typ = stepinfo(H,'RiseTimeLimits',[0.00,0.60]);
19
20 fprintf(fp, 'Given:\r\nR_low: %.3f Ohms\r\nR_max = %.3f', R_low, R_high);
21 fprintf(fp, ' Ohms\r\nC = %.3f pF\r\n \r\n', C*1e12);
22
23 fprintf(fp, 'Low end dead time:\r\nTypical:%snS \r\n', S_typ.RiseTime*1e9);
24 fprintf(fp, 'Min:%snS \r\nMax:%snS', S_min.RiseTime*1e9, S_max.RiseTime*1e9);
25
26 H = (1/(R_high*C))/(s+(1/(R_high*C)));%Filter transfer function
27
28 S_min = stepinfo(H,'RiseTimeLimits',[0.00,0.52]);
29 S_max = stepinfo(H,'RiseTimeLimits',[0.00,0.68]);
30 S_typ = stepinfo(H,'RiseTimeLimits',[0.00,0.60]);
31
32 fprintf(fp, '\r\n \r\nHigh end dead time:\r\nTypical:%snS', S_typ.RiseTime*1e9);
33 fprintf(fp, ' \r\nMin:%snS \r\nMax:%snS', S_min.RiseTime*1e9, S_max.RiseTime*1e9);

```

Listing 17: V12switcher.m

```

1 %Author: Nathaniel Rohrick

```



```

2 %Filename: V12switcher.m
3 %Date: March 30, 2017
4 %Description: Design of 12V buck SMPS using TPS54360
5
6 clc;clear;
7 filep = fopen('V12switcher.txt', 'w');
8
9 Rdc = 0.0488;           %Inductor resistance, assume 25m0hm
10 Vout = 12;            %Output voltage
11 io = 1.5;             %Nominal current value
12 icl = 3.5;           %Current limit
13 Vin = 24;             %Input voltage
14 Vin_max = 48;         %Maximum expected input voltage
15 Vd = 0.3;             %Forward diode voltage (assumption)
16 Vf = 0.8;            %Internal forward voltage drop
17 Cd = 300e-12;        %Diode capacitance estimate
18 Rds_on = 0.092;      %Maximim internal rdson from datasheet
19 Ton_min = 135e-9;    %Minimum controllable on time from datasheet
20 Vref = 0.8;          %internal reference voltage
21 tr = 4.9e-9;         %estimated rise time of internal gate drive
22 Qg = 3e-9;           %estimated gate charge of internal fet
23 Iq = 146e-6;         %queiscent current of chip
24 f_div = 8;           %Frequency divider of control loop
25 Vsc = 0.1;           %Short circuit output voltage
26 Kind = 0.3           %Allowable ripple current as fraction of output current
27 f_maxskip = (1/Ton_min) * (((io*Rdc)+Vout+Vd)/(Vin_max-(io*Rds_on)+Vd))
28 f_shift = (f_div/Ton_min) * (((icl*Rdc)+Vsc+Vd)/(Vin_max-(icl*Rds_on)+Vd))
29 dI = 0.5;            %Allowable change in load current
30 dV = Vout*0.01;      %Allowable change in load voltage
31 Ioh = 1.5;           %Output current under heavy load
32 Iol = 0.9;           %Output current under light load
33 Ihys = 3.4e-6;      %hysteresis current specified in datasheet
34 Ienin = 1.2e-6;     %Enable input current
35 Vstart = 20;         %PSU starts at input voltage of 20V
36 Vstop = 18;          %PSU stops at input voltage of 16V
37 Ven = 1.2;           %Enable voltage level without hysteresis
38 gmps = 12;           %COMP to SW current transconductance
39 gmea = 250e-6;      %error amplifer transconductance
40
41 %Pick 10^log10x below lowest frequency found above.
42 if (f_maxskip > f_shift)
43     fsw = roundn(f_shift - 10^floor(log10(f_shift)), floor(log10(f_shift)));
44 else
45     fsw = roundn(f_maxskip - 10^floor(log10(f_maxskip)), floor(log10(f_maxskip)));
46 end
47
48 RT = rpv((92417 / ((fsw/1000)^0.991))*1000);
49 RT = RT(1,1);       %R3
50
51 %Inductor value calculations
52 Lo_min = ((Vin-Vout)/(io*Kind))*((Vout)/(Vin*fsw));%L1
53 Lo_min = 33e-6;     %chose 513-1351-1-ND
54 Irip = ((Vout*(Vin - Vout))/(Vin*Lo_min*fsw));
55 Il_rms = sqrt((io^2)+((1/12)*(((Vout*(Vin-Vout))/(Vin*Lo_min*fsw))^2)));

```

```

56 Il_pk = io + (Irip/2);
57
58 %Capacitor value calculations
59 Co1 = ((2*dI)/(fsw*dV));
60 Co2 = Lo_min*(((Ioh^2)-(Iol^2))/(((Vout+dV)^2)-(Vout^2)));
61 Co3 = (1/(8*fsw))*(1/(dV/Irip));
62 Co = 8*max([Co1 Co2 Co3]);%C6/C7
63 Co = 44e-6;%chose 2 22u in parallel HHXA500ARA220MF61G
64 Resr = (dV/Irip);%C6/C7 ESR
65 Resr = 40e-3;%chosen capacitor HHXA500ARA220MF61G in parallel
66 Icout_rms = (Vout/sqrt(12))*((Vin-Vout)/(Vin*Lo_min*fsw));%C6/C7 irip rms
67
68 %Diode value calculations
69 Pd = (((Vin-Vout)*io*Vd)/Vin)+((Cd*fsw*((Vin+Vd)^2))/2);
70
71 %Input capacitor value
72 Cin = 4.7e-6;%C1/C2
73 %input rms ripple current %C1/C2 rip rms
74 I_ic = io*sqrt((Vout/Vin)*((Vin-Vout)/Vin));
75 dVin = (io*0.25)/(Cin*fsw);%input ripple voltage
76
77 %Bootstrap capacitor value
78 Cboot = 0.1e-6;%specified in datasheet C4
79
80 %Under and overvoltage lockout resistor selection
81 Ruvlo1 = rpv((Vstart - Vstop) / Ihys);
82 Ruvlo1 = Ruvlo1(1,1);%R1
83 Ruvlo2 = rpv(Ven / (((Vstart - Ven)/Ruvlo1)+Ienin));
84 Ruvlo2 = Ruvlo2(1,1);%R2
85
86 %Output feedback resistor selector
87 Rls = 10e3; %pick 10k for low side resistor R6
88 Rhs = rpv(Rls * (Vout - Vf) / Vf);
89 Rhs = Rhs(1,1);%R5
90
91 %Compensation values for voltage control loop
92 fp = io / (2*pi*Vout*Co);
93 fz = 1 / (2*pi*Resr*Co);
94 Fco1 = sqrt(fp*fz);
95 Fco2 = sqrt(fp*(fsw/2));
96 fco = min(Fco1,Fco2);
97 R4 = rpv(((2*pi*fco*Co)/gmgs)*(Vout/(Vref*gmea)));
98 R4 = R4(1,1);
99 C5 = 1/(2*pi*R4*fp);
100 C8_1 = (Co*Resr) / R4;
101 C8_2 = 1/(R4*fsw*pi);
102 C8 = max(C8_2, C8_1);
103
104 %Power dissipation estimates for RPS54360
105 Pcond = (io^2)*Rds_on*(Vout/Vin);
106 Psw = Vin*fsw*io*tr;
107 Pgd = Vin*Qg*fsw;
108 Pq = Vin*Iq;
109 Pt = Pcond+Pq+Pgd+Psw;

```

```

110
111 fprintf(filep, 'This file computes component values for TPS54360DDA');
112 fprintf(filep, ', refer to\ndatasheet for more information\r\n');
113 fprintf(filep, '\n\nR1 = %.2f\r\nR2 = %.2f\r\n', Ruvlo1, Ruvlo2);
114 fprintf(filep, 'R3 = %.2f\r\nR4 = %.2f\r\n', RT, R4);
115 fprintf(filep, 'R5 = %.2f\r\nR6 = %.2f\r\n', Rhs, Rls);
116 fprintf(filep, 'C1/C2 = %.2fuF\r\nC4 = %.2fuF\r\n', Cin*1e6, Cboot*1e6);
117 fprintf(filep, 'C5 = %.2fnF\r\n' C5*1e9);
118 fprintf(filep, 'C6/C7 = %.2fuF\r\nC8 = %.2fnF\r\n', Co*1e6, C8*1e9);
119 fprintf(filep, 'L = %.2fuH\r\nP Total = %.2f', Lo_min*1e6, Pt);

```

Listing 18: GATE_DRV_DESIGN.m

```

1 %Author: Nathaniel Rohrick
2 %Date: February 28, 2017
3 %Description: Creates a list of component values needed for TI's UCC27714
4 %               gate driver IC
5
6 fp = fopen('gate_drive.txt', 'w');
7
8 Qg = 35e-9;           %11nC gate charge AUIRF7640S2CT-ND from digikey
9 Rg = 3.5;            %Intrinsic gate resistance is 3.5Ohm from ds
10
11 fsw = 500e3;         %500 kHz switching frequency
12 Vhv = 24;           %High voltage supply
13 Iqdd = 1050e-6;     %Quiescent current of gate driver Vdd to Vss
14 Iqbs = 300e-6;     %Quiescent current of HB-HS supplies of gate driver
15 Ibl = 20e-6;        %Bootstrap leakage current
16 Vf = 0.3;          %Boot diode Vf
17 Vdd = 12;           %Gate drive voltage supply
18 Cg = Qg / (Vdd - Vf); %Equivalent gate capacitance
19 Cboot = 10 * Cg;    %Bootstrap cap cant drop 10% in voltage, spec
20                    %cap to be 10x gate capacitance
21
22 Cvdd = 10 * Cboot;  %Vdd capacitor recommended by TI to be 10x Cboot
23
24 Rbias = 5;          %To allow Vdd pins voltage to ramp longer than 50uS
25                    %This is to prevent error logic spikes on O/P
26 Rboot = 2.2;        %Recommended value between 2.2-10, pick minimum
27 Idbootpk = (Vdd - Vf) / Rboot; %Max current boot diode sees on startup
28
29 Pqc = Vdd * (Iqdd + Iqbs); %Quiescent current power dissipation
30 Pibl = ((Vdd+Vhv) - Vf) * Ibl * 0.5; %Static losses due to HB leakage
31                    %current at 50% duty cycle PWM
32 Pq1q2 = 2 * Vdd * Qg * fsw; %Primary power dissipation element turning on
33                    %and off fets.
34 Plvlshft = (Vdd+Vhv) * (0.5e-9) * fsw; %Level shift power dissipation
35                    %assuming 0.5nC of parasitic charge
36 P_INT = Plvlshft + Pq1q2 + Pibl + Pqc; %Total internal power dissipation
37
38 %Find ripple current of gate driver
39 %Assume maximum allowable current
40 T = 1/fsw;          %Period of switching waveform
41 I = (Vdd - Vf)/Rg; %Max current from gate driver

```

```

42 Tc = Qg / I;           %Charge up time
43
44 t = 0:(T/10e3):T;
45 Iwv1 = I*heaviside(t - (T/2)) - I*heaviside(t - (T/2 + Tc));
46 Iwv2 = -I*heaviside(t - (T-Tc)) + I*heaviside(t - T);
47 Iwv = Iwv1 + Iwv2;
48 RMS_Iwv = sqrt((mean(Iwv.^2)));
49
50 RMS_TOTAL = 2 * RMS_Iwv;           %2 drivers per chip
51
52
53
54 fprintf(fp, 'Cboot is: %.4fnF\r\nRboot is: %.4f0hms\r\n', (Cboot*1e9), Rboot);
55 fprintf(fp, '\r\nInternal Power Dissipation Tabulated Below\r\n');
56 fprintf(fp, 'Total internal Power dissipation: %.5fW\r\n', P_INT);
57 fprintf(fp, 'Switching losses: %.5fW\r\n', Pq1q2);
58 fprintf(fp, 'Level shifting losses: %.5fW\r\n', Plvlshft);
59 fprintf(fp, 'Quiescent current losses %.5fW\r\n', (Pqc + Pibl));
60 fprintf(fp, '\r\nRipple Current Rating for bulk decoupler: %.5fA', RMS_TOTAL);
61
62 fclose(fp);

```

6.4 Bill of Materials

6.4.1 BOM billed to BCIT

Sheet1

Group No.	Supplier	Part URL	Description	Quantity	Unit Cost
16	Adafruit	https://www.adafruit.com/product/447	MicroSD card breakout board	1	9.95
16	Adafruit	https://www.adafruit.com/product/447	MicroSD card breakout board	1	7.5
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	Stereo audio DAC	1	8.54
16	Adafruit	https://www.adafruit.com/product/1100	SMT breakout board for DAC	1	4.95
16	Sparkfun	https://www.sparkfun.com/products/14920	Rotary encoder	1	2.95
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	Ceramic bypass cap (0.1uF)	1	0.28
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	Tantalum bypass cap (10uF)	1	0.88
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	Audio op-amp (OPA2134PA)	1	6.16
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	1% 10k resistor	6	0.14
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	Ceramic cap (100pF)	2	0.3
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	Ceramic cap (680pF)	2	0.43
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	Ceramic cap (1500pF)	2	0.51
16	Digikey	http://www.digikey.com/product-detail/en/100000012/100000012-ND	DC blocking cap (1000uF)	2	0.51
16	Sparkfun	https://www.sparkfun.com/products/14920	TRRS 3.5mm breakout	1	3.95
			total		

Page 1

Figure 18: Components used in final design

6.4.2 Class-D Amplifier BOM

Name	Manufacturer	Description	Digikey P/N	Type	Value	Package	Unit Cost	Design Quantity	Purchase Quantity	Total Cost
TL50M12CKVURG3	TI	12V Regulator	296-21601-1-ND	IC		14SOIC	1.42	1		\$ 1.42 C
UCC27714D	TI	Gate Driver +/- 4A	296-42629-5-ND	IC		14SOIC	4.54	4		\$ 18.16 C
LM2937	TI	5V Regulator	LM2937ESX-5.0NOPBCT-ND	IC		DPAK	1.87	1		\$ 1.87 C
TLV3501, TLV3502	TI	Comparator	296-43612-1-ND	IC		8-SOIC	5.57	2		\$ 11.14 C
OPA365, 2365	TI	Op-Amp	296-31704-1-ND	IC		8-SOIC	3.92	2		\$ 7.84 C
PTD90	Bourns Inc.	2 Ganged Log Pot	PTD902-2015K-A503-ND	R	50k	Through-Hole	2.85	2		\$ 5.70 C
Shunt Jumper	3M	Female Jumper	3M9580-ND	JP		Socket	0.14	6		\$ 0.84 C
Pin Header	3M	Male 2-Pin Header	3M9447-ND	JP		Through-Hole	0.16	6		\$ 0.96 C
10k Ohm Resistor	Yageo	0.1% 10k Resistor	YAG2329CT-ND	R	10k		1206	0.51	5	\$ 2.55 C
FDY302N2	Fairchild	Logic NMOS	FDY302NZCT-ND	NMOS	20V	SC89		0.47	8	\$ 3.76 C
CD74AC14	TI	6x Inverting Schmitt Trigger	296-1981-1-ND	IC		SOIC 14	0.89	2		\$ 1.78 C
200k Ohm Resistor	Yageo	1% 200k Resistor	311-200KFRCT-ND	R	200k		1206	0.1	1	\$ 0.10 C
10k Ohm Resistor	Yageo	1% 10k Resistor	311-10.0KFRCT-ND	R	10k		1206	0.1	21	\$ 2.10 C
5.9k Ohm Resistor	Yageo	1% 5.9k Resistor	311-5.90KFRCT-ND	R	5.9k		1206	0.1	1	\$ 0.10 C
8.45k Ohm Resistor	Yageo	1% 8.45k Resistor	311-8.45KFRCT-ND	R	8.45k		1206	0.1	1	\$ 0.10 C
1uF Capacitor	KEMET	10% 1uF MLCC Capacitor	399-1254-1-ND	C	1uF 15V		1206	0.17	8	\$ 1.36 C
0.1uF Capacitor	KEMET	10% 0.1uF MLCC Capacitor	399-9305-1-ND	C	0.1uF 15V		1206	0.11	9	\$ 0.99 C
4.7uF Capacitor	KEMET	10% 4.7uF MLCC Capacitor	399-3524-1-ND	C	4.7uF 15V		1206	0.31	5	\$ 1.55 C
22uF Capacitor	United Chemi-Con	20% 22uF Electrolytic Capacitor	HHXA500ARA220MF61G	C	22uF 50V	F61 SMT		1.41	4	\$ 5.64 C
N-CH MOSFET	Infineon	100V 36nC NMOS	IRF6644TRPBFCT-ND	MOSFET	36nC 100V	DirectFET		2.95	8	\$ 23.60 C
1uF Capacitor	KEMET	10% 1uF MLCC Capacitor	399-8147-1-ND	C	1uF 50V		1206	0.23	11	\$ 2.53 C
0.1uF Capacitor	KEMET	10% 0.1uF MLCC Capacitor	399-1249-1-ND	C	0.1uF 50V		1206	0.1	8	\$ 0.80 C
MBRS1100T3G Diode	ON Semiconductor	1A Shottky Diode	MBRS1100T3GOSCT-ND	D	1A 100V	SMB 403A-03		0.4	12	\$ 4.80 C
MBR0530T1G Diode	ON Semiconductor	0.5A Shottky Diode	MBR0530T1GOSCT-ND	D	0.5A 30V	SOD-123		0.36	8	\$ 2.88 C
F6505CT-ND	Littlefuse	200W TVS	SPHV12-01ETG-C	TVS	200W 25V	SOD-882		0.4	8	\$ 3.20 C
SMCJ60CA	Littlefuse	1.5kW TVS	SMCJ60CALFCT-ND	TVS	1.5kW 100V	DO-214AB		0.62	8	\$ 4.96 C
EEV-FK1J471M	Panasonic	470uF Electrolytic Capacitor	PCE3485CT-ND	C	470u 63V	SMT		1.88	6	\$ 11.28 C
UVR1J472MRD6	Nichicon	4.7mF Electrolytic Capacitor	493-1134-ND	BFC	4.7mF 63V	Through-Hole		4.61	2	\$ 9.22 C
165EV470M10X10.5	Rubycon	470uF Electrolytic Capacitor	1189-2403-1-ND	C	470uF 16V	SMD		0.8	0	\$ - C
25TKV470M10X10.5	Rubycon	470uF Electrolytic Capacitor	1189-2072-1-ND	C	470uF 25V	SMD		1.14	2	\$ 2.28 C
OSTTC040162	On Shore Technology	4 Port Screw Terminal	ED2602-ND	CONN		Through Hole		0.79	1	\$ 0.79 C
OSTTC022162	On Shore Technology	2 Port Screw Terminal	ED2609-ND	CONN		Through Hole		0.42	2	\$ 0.84 C
SJ-2524-SMT-TR	CUI Inc.	4 Terminal Stereo Jack	CP-2524SCT-ND	CONN		SMD		0.98	1	\$ 0.98 C
QBLP615-IB	QT Brighttek (QTB)	Blue LED	1516-1072-1-ND	D	Blue D 3.1V		1206	0.5	1	\$ 0.50 C
QBLP615-IG	QT Brighttek (QTB)	Green LED	1516-1073-1-ND	D	Green D 3.1V		1206	0.5	1	\$ 0.50 C
QBLP615-R	QT Brighttek (QTB)	Red LED	1516-1076-1-ND	D	Red 2V		1206	0.41	1	\$ 0.41 C
ST141D00	E-Switch	SPST Toggle Switch	EG4810-ND	SW	20A 125V	Panel (Through Hole)		4.28	1	\$ 4.28
100 Ohm Resistor	Yageo	1% 100 Resistor	YAG3804CT-ND	R			100	1206	0.1	\$ 0.60 C
154 Ohm Resistor	Yageo	1% 154 Resistor	YAG3814CT-ND	R			154	1206	0.1	\$ 0.10 C
100pF Capacitor	Würth	5% 100pF MLCC	732-7868-1-ND	C	100pF		1206	0.35	5	\$ 1.75 C
1k Pot	Copal Electronics Inc.	1k Potentiometer	ST4ETA102CT-ND	R POT	1k	SMD		1.32	4	\$ 5.28
1uF Film Cap	KEMET	5% 1uF Film Capacitor	R82EC4100DQ70J	C	1uF 63V	Through Hole		1.06	4	\$ 4.24
33uH	Eaton	15% 33uH Inductor	513-1351-1-ND	L	33uH 4.42A	SMD		3.36	4	\$ 13.44
2R2	Vishay	5% 2.20hm Film Resistor	541-2.2RACT-ND	R	2.20hm		2512	0.59	4	\$ 2.36 C
5R5	Vishay	5% 50hm Film Resistor	541-5.1R8CT-ND	R	50hm		2512	0.75	4	\$ 3.00 C
TOTAL								202		\$ 172.58

Figure 19: Components needed for class-D amplifier